

## **ELE 215.3 Network Theory (3-1-2)**

### **Evaluation:**

	Theory	Practical	Total
Sessional	30	20	50
Final	50	-	50
Total	80	20	100

### **Course Objectives:**

The purpose of the course is to provide the knowledge of network equations and the behavior of network. Moreover, it provides in-depth knowledge to develop one-port and two port networks with given network functions.

### **Course Contents:**

- 1. Review of Network Analysis** (2 hrs)  
1.4 Mesh and Nodal analysis
- 2. Circuit Differential Equations (Formulation and Solutions)** (5 hrs)  
2.10 The differential operator  
2.11 Operational impedance  
2.12 Formulation of circuit differential equations  
2.13 Complete response (transient and steady state) of first order differential equations with or without initial conditions
- 3. Circuit Dynamics** (7 hrs)  
3.7 First order RL and RC circuits  
3.8 Complete response of RL and RC circuit to sinusoidal input  
3.9 RLC circuit  
3.10 Step response of RLC circuit  
3.11 Response of RLC circuit to sinusoidal inputs  
3.12 Damping factors and Damping Coefficients.
- 4. Review of Laplace Transform** (5 hrs)  
4.7 Definition and properties  
4.8 Laplace transform of common forcing functions  
4.9 Initial and final value theorem  
4.10 Inverse Laplace transform  
4.11 Partial fraction expansion  
4.12 Step response of RL, RC and RLC circuit

- 4.13 Sinusoidal response of RL, RC and RLC circuits  
4.14 Exponential response of RL, RC and RLC circuits

**5. Transfer Functions (4 hrs)**

- 5.7 Transfer functions of network system  
5.8 Poles and Zeros  
5.9 Time domain behavior from pole-zero locations  
5.10 S Routh' - Hurwitz's stability Criteria

**6. Fourier Series and Transform (4 hrs)**

- 6.8 Evaluation of Fourier coefficients for periodic non-sinusoidal waveform  
6.9 Fourier Transform  
6.10 Application of Fourier transforms for non-periodic waveforms

**7. Frequency Response of Network (7 hrs)**

- 7.10 Magnitude and phase responses  
7.11 Bode plots and its applications  
7.12 Concept of ideal and non-ideal low pass, high pass, band pass, and band reject filters

**8. One-port Passive Network (7 hrs)**


- 8.12 Properties of one-port passive network  
8.13 Positive Real Function  
8.14 Properties of RL, RC and LC network  
8.15 Synthesis of RL, RC and LC networks using Foster's and Cauer's method  
8.16 Properties of RLC one-port network

**9. Two-port Passive Network (7 hrs)**

- 9.8 Properties of two-port network  
9.9 Reciprocity and symmetry  
9.10 Short circuit and Open circuit parameters  
9.11 transmission parameters  
9.12 Hybrid parameter  
9.13 Relation and transformations between sets of parameters  
9.14 Equivalent T and  $\pi$  section representation


**Laboratory:**

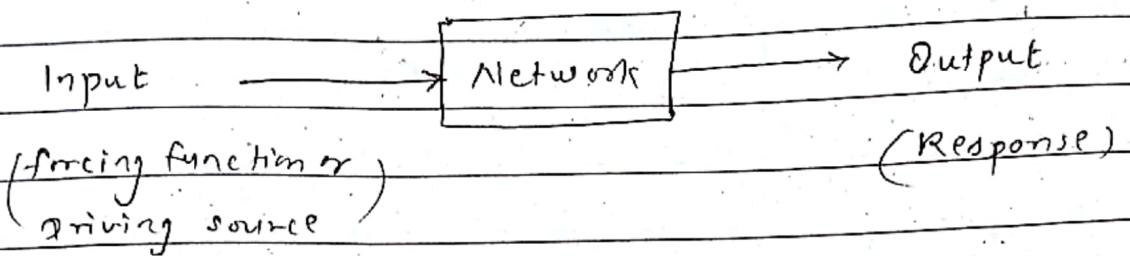1. Transient and steady state responses of first order Passive network
  - 1.1 Measurement of step, impulse and ramp response of RC and RL circuit using oscilloscope
  - 1.2 Measurement of sinusoidal response of RC and RL circuit using oscilloscope



### \* Some Basic Forcing Functions.

#### 1. Unit step function

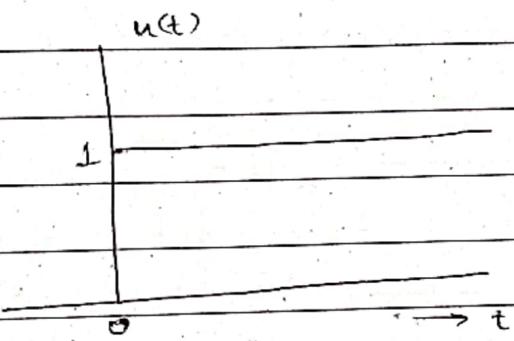


$$u(t) = 1, \quad t > 0 \\ = 0, \quad t < 0$$

#### 2. Step function


can have any value for positive half side.  
 e.g. 10V, 50V etc.

#### 2. Ramp function

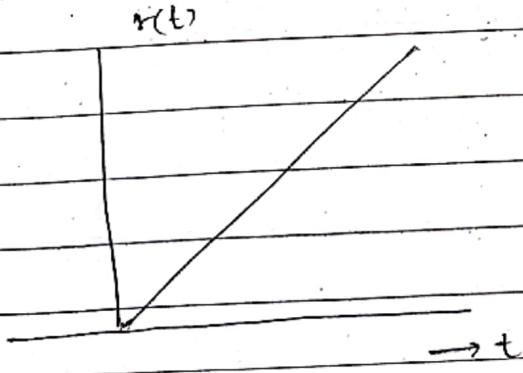


$$r(t) = t \quad t > 0 \\ = 0 \quad t < 0$$


## 3. Exponential function.

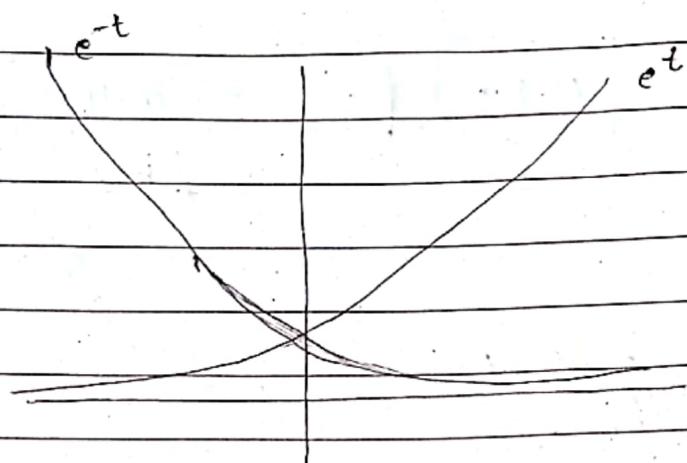

## 4. Sinusoidal function

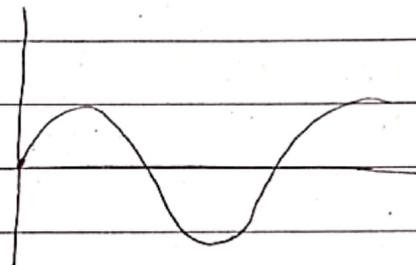
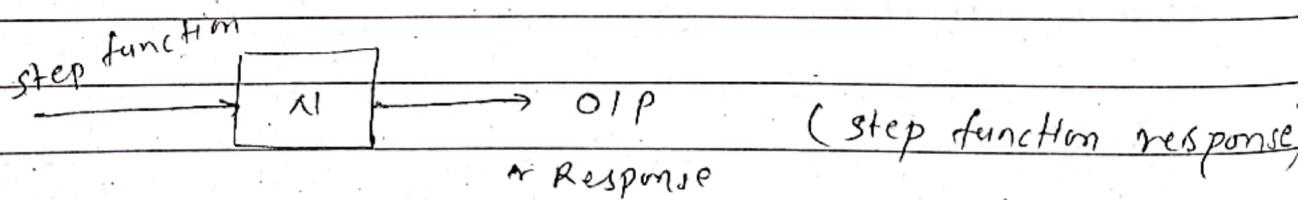
$$v = V_m \sin(\omega t), \quad v = V_m \cos(\omega t)$$



\* Passive elements and their relations

### 1) Resistor ( $R$ )

symbol -  $R$

unit - ohm ( $\Omega$ )

$$V(t) = i(t) R$$

$$\Rightarrow R = \frac{V(t)}{i(t)}$$

$$i(t) = \frac{V(t)}{R}$$

The resistor doesn't store any current or voltage just after switching.

### 2) Inductor ( $L$ )

symbol -  $L$

unit - Henry ( $H$ )

$$mH \text{ (millihenry)} = 10^{-3} H$$

$$V \propto \frac{d i(t)}{dt}$$

KVL

$$V = L \frac{d i(t)}{dt} ; \text{ voltage across inductor.}$$

Inductance.

$$d i(t) = \frac{V}{L} dt$$

Integration,

$$i(t) = \frac{1}{L} \int V(t) dt ; \text{ current through inductor.}$$

$i(t)$

Inductor stores the current for a very small time just after switching:

$$i(0^-) = \cancel{i(0^+)} i(0^+)$$

### 3.7 Capacitor (C)

Symbol:  $\rightarrow C$

Unit  $\rightarrow$  Farad (F)

$\mu F$  (micro Farad)  $\rightarrow 10^{-6} F$ .

$q(t) = C V(t)$ ; charge

$$V(t) = \frac{q(t)}{C}$$

$$I(t) = \frac{dq(t)}{dt}$$

$$dq(t) = i(t) dt$$

$$q(t) = \int i(t) dt$$

$$V(t) = \frac{1}{C} \int i(t) dt ; \text{ voltage across capacitor.}$$

Differentiating.

$$\frac{dV(t)}{dt} = \frac{1}{C} i(t)$$


$$i(t) = C \frac{dV(t)}{dt} ; \text{ current through capacitor.}$$

Capacitor stores the charge or voltage just after switching for very few seconds.



$$V(0^-) = V(0^+) \quad \text{or} \quad q(0^-) = q(0^+)$$

## \* Switching Function


(1)

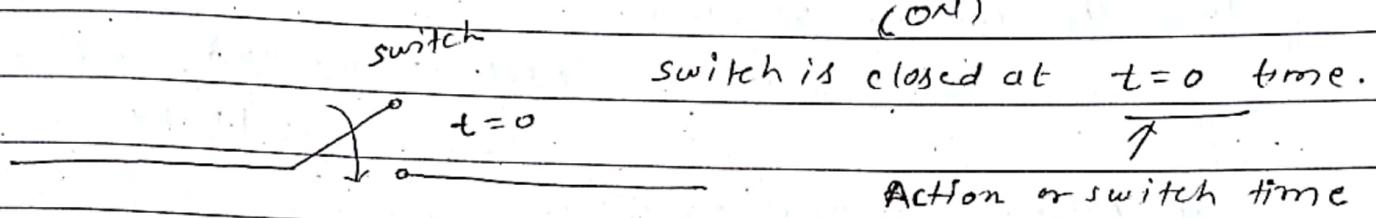

(2)

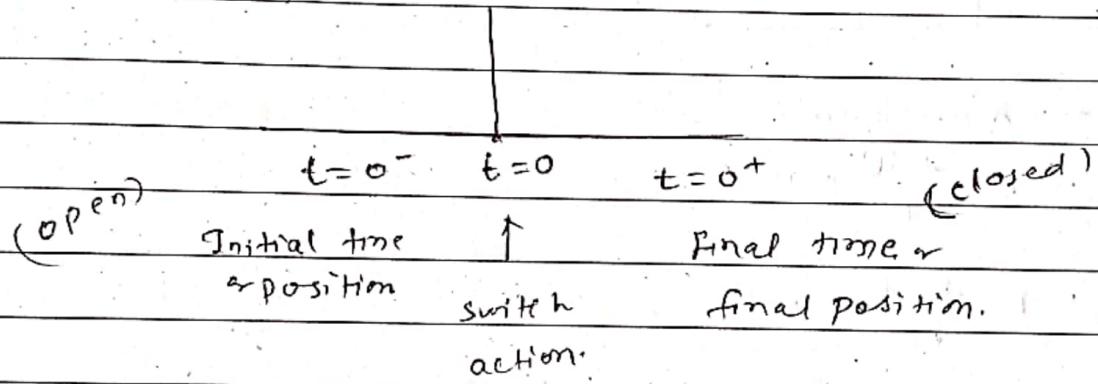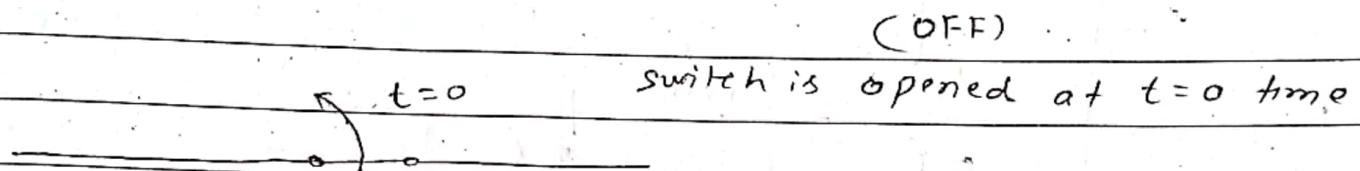
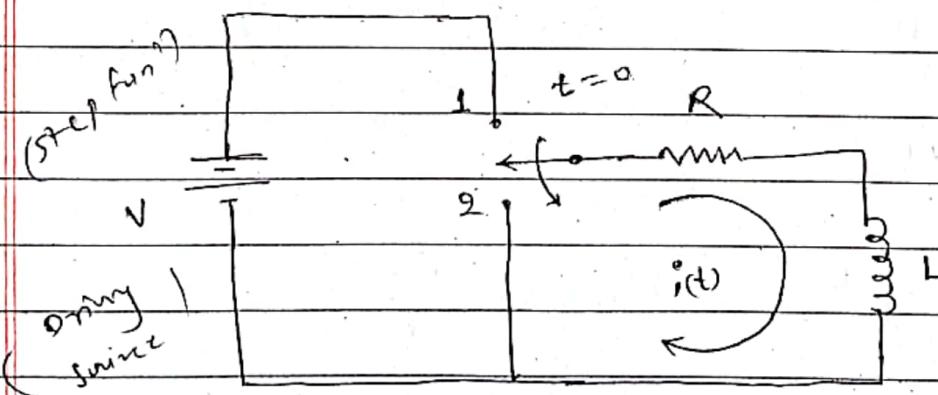
## \* Step Function Response of R-L Series Circuit




The switch is moved from position 1 to 2 at  $t=0$   
Find the current response.

Response ~~initial~~  $\rightarrow$  Final  
position.

Sol'

At  $t=0$ , the final circuit is

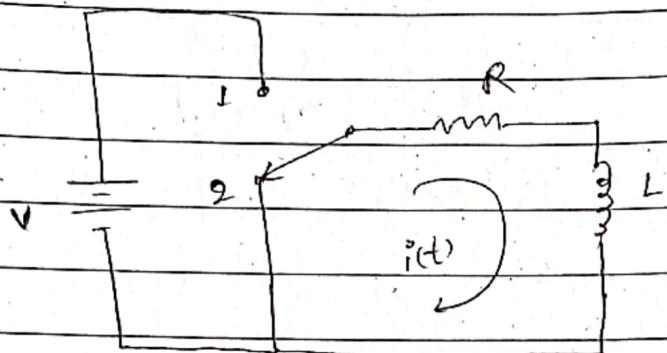

Applying mesh analysis.

$$-R i(t) - L \frac{di(t)}{dt} = 0$$

$$R i(t) + L \frac{di(t)}{dt} = 0$$

$L \frac{di(t)}{dt} + R i(t) = 0$ ; First order homogeneous differential equation.

$$\frac{di(t)}{dt} + \frac{R}{L} i(t) = 0$$

$$\frac{di(t)}{dt} = -\frac{R}{L} i(t)$$


$$\frac{di(t)}{i(t)} = -\frac{R}{L} dt$$

$$-\frac{1}{L} \frac{R}{L} t$$

$$i(t) = K e^{-\frac{R}{L} t}$$

General solution.

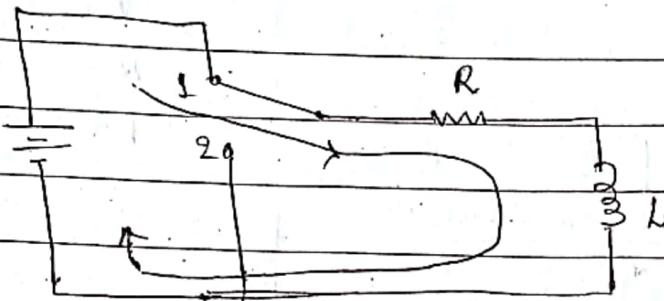To find  $K$ , we use initial position ckt.



$$i(0-) = \frac{V}{R} \text{ (due to no reactance)}$$

Put in general solution,

$$\frac{v}{R} = K \cdot e^{-\frac{R}{L}t}$$

$$\Rightarrow K = \frac{V}{R}$$

$$\text{Now, } i(t) = \frac{V}{R} e^{-\frac{R}{L}t}$$

particular solution.

H/W

$V = 20V$

$R = 2 \Omega$

$L = 1H$


switch position 1 to 2

switch is position manual

from 1 to 2 at

$t = 0$ . Find on

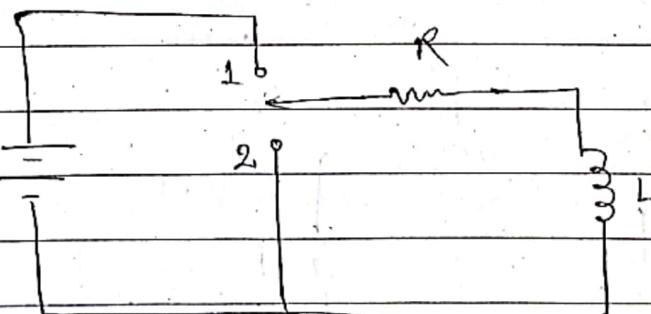Also find the voltage across inductor. current response.  $\rightarrow$




$\frac{dV}{dt}$ At  $t=0$ , C.R.T of final position is.

$$V = 20V$$

$$R = 2\Omega$$

$$L = 1H$$

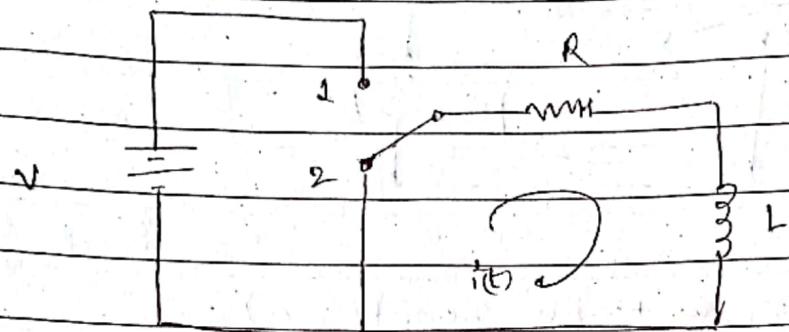

Now applying mesh analysis, we have

$$-2i_1 - \frac{di_1}{dt} = 0$$

$$2i_2 + \frac{di_2}{dt} = 0$$


$$\therefore \frac{di_1}{dt} = -2i_1$$

$$\therefore \frac{di_2}{dt} = -2i_2$$

$$\Rightarrow i_1(t) = K e^{-2t} \quad \text{--- (i)}$$

To find  $i_2$ , we use initial position of C.R.T

i.e.

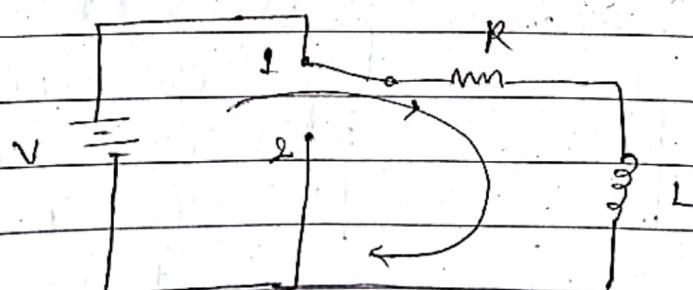

$$\text{Hence, } i(0^+) = \frac{V}{R} = \frac{20}{2} = 10 \text{ Amp.}$$

since,  $i(0^-) = i(t)$  at  $t = 0$ .

from ①

$$10 = K e^{-2t=0}$$

$$\Rightarrow K = 10$$

$$\text{So, } i(t) = 10e^{-2t} \quad \text{--- (2)}$$

Now, voltage across inductor.

$$V(t) = L \frac{di(t)}{dt}$$

$$= 1 \cdot \frac{d}{dt} 10 e^{-2t}$$

$$= 10 \frac{d}{dt} e^{-2t}$$


$$= 10 \cdot e^{-2t} \times -2$$

$$V(t) = -20 e^{-2t}$$

\* Step function Response of RC series circuit.


switch is moved from position 1 to 2 at  $t=0$ .

Find the current response at 5 second.

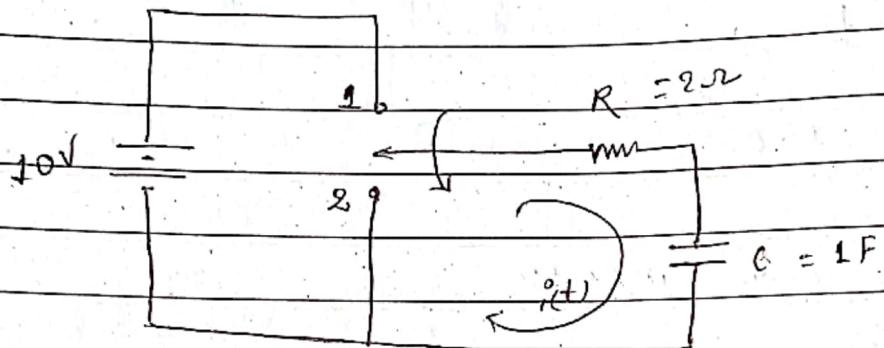

Soln

At  $t=0$ , final circuit

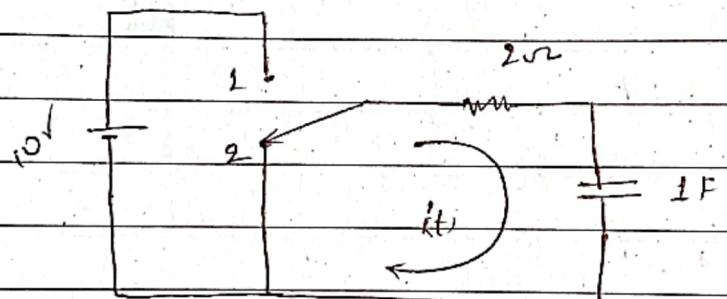

Applying KVL

$$-R i(t) - \frac{1}{C} \int i(t) dt = 0$$

$$-R i(t) + \frac{1}{C} \int i^2(t) dt = 0$$

$$-2 i(t) + \frac{1}{C} \int i^2(t) dt = 0 \quad \text{--- (1)}$$

Differentiating both sides w.r.t  $t$

$$2 \cdot \frac{d i(t)}{dt} + i(t) = 0$$

$$\frac{d i(t)}{dt} + \frac{1}{2} i(t) = 0$$

First order differential eq? (Homogeneous)

$$\frac{d i(t)}{dt} = -\frac{1}{2} i(t)$$

$$\frac{d i(t)}{i(t)} = -\frac{1}{2} dt$$

Integration.  $\int_{i_0}^{i(t)} \frac{1}{i} di = -\frac{1}{2} t$

$$i(t) = K e^{-\frac{1}{2} t}$$


Initially

capacitor stores 10V

voltage as initial voltage

and capacitor does not change

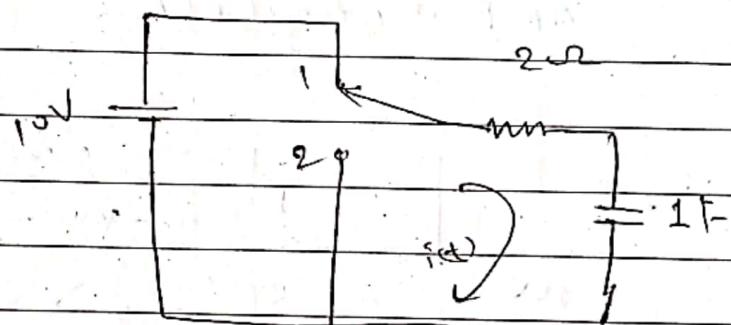its initial value instantly just after switching.



From qn ①

$$2 i(0^-) + 10 = 0$$

$$i(0^-) = -5 \text{ Amp.}$$

At 5 seconds  $\rightarrow$   
 $i(t) = -5 e^{-\frac{1}{2} t}$

$$i(t) = -5 e^{-\frac{1}{2} t} \text{ Amp.}$$

putting in general solution


$$-5 = K e^{-\frac{1}{2} * 0}$$

$$K = -5$$

$$-5 e^{-\frac{1}{2} t}$$


$$\Rightarrow i(t) = -5 e^{-\frac{1}{2} t}$$

which is particular solution.

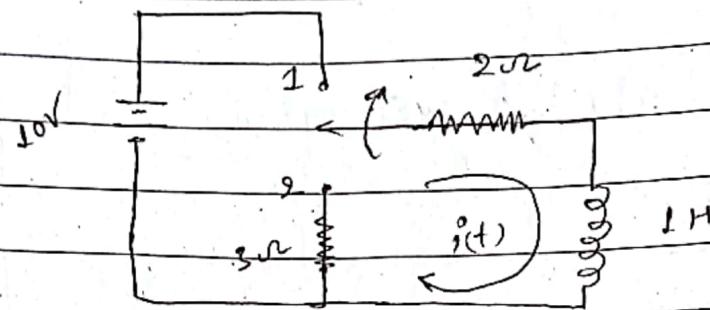

switch is moved from position 2 to 1 at  $t=0$ .  
Find the current response.

Sol: At  $t=0$ , final circuit,

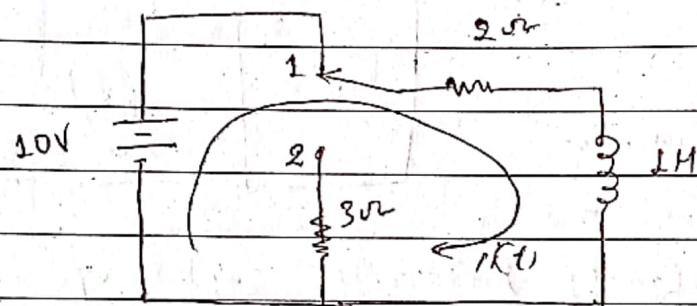

Applying mesh analysis, or KVL

$$-2i(t) - L \cdot \frac{di(t)}{dt} + 10 = 0$$

$$\therefore L \frac{d^2i(t)}{dt^2} + 2i(t) = 10$$

1st order ~~homogeneous~~ diff. eq? (non-homogeneous)

H.P.N,

$$\rho = 2, Q = 10$$

$$\frac{d i(t)}{dt} + p i(t) = q$$

Date \_\_\_\_\_  
Page \_\_\_\_\_

$$i(t) = e^{-pt} \int q \cdot e^{pt} dt + k e^{-pt}$$

now:

$$i(t) = e^{-2t} \int 10 e^{2t} dt + k e^{-2t}$$


$$i(t) = 10 e^{-2t} \cdot \frac{e^{2t}}{2} + k e^{-2t}$$

$$i(t) = 5 + k e^{-2t} \quad \text{General Solution.}$$

Initial ckt.

position 2  $\rightarrow$  5  $\rightarrow$  3  $\rightarrow$  4  $\rightarrow$

voltage source  $E_0$  connect

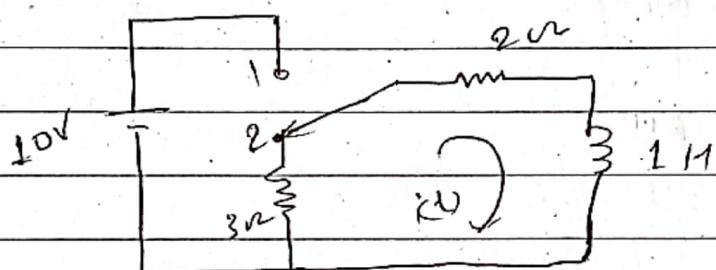

$\frac{di}{dt}$  current  $i(0^-) = 0$

i.e.  $i(0^+) = 0$

from general solution,

$$0 = 5 + k e^{-2 \cdot 0}$$

$$0 = 5 + k \times 1$$

$$\Rightarrow k = -5$$


Required solution is

$$i(t) = 5 - 5e^{-2t} \quad \text{which is particular soln.}$$

steady state solution

Transient state solution.

\* PU

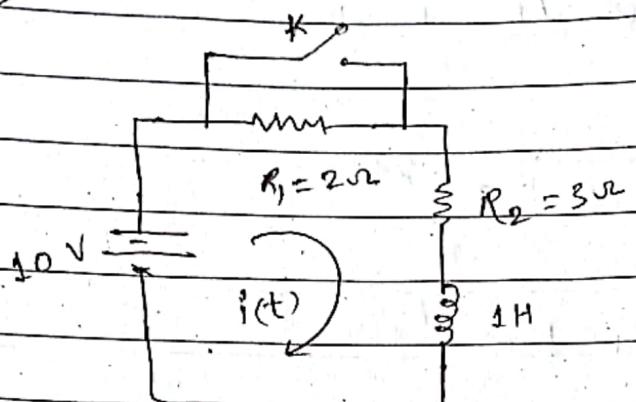


(a) Switch is closed at  $t=0$   
Find the current response

(b) Switch is opened at  $t=0$   
Find the current response

(a)

Final ckt.

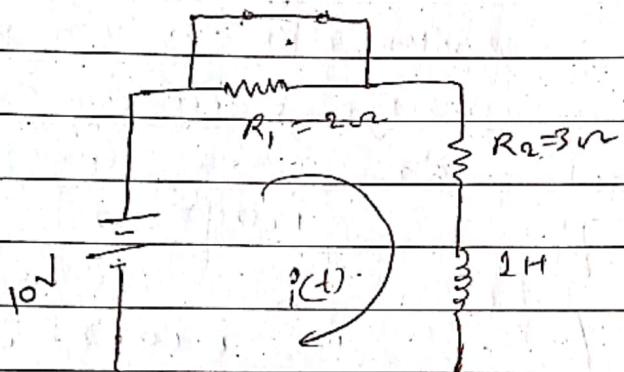

Applying mesh analysis.

$$-3i(t) - \frac{d}{dt}i(t) + 10 = 0$$

$$\frac{d^2i(t)}{dt^2} + 3i(t) = 10$$

which is non-homogeneous 1st order diff eq

so we

$$p = 3$$

$$q = 10$$


$$Qn \quad i(t) = e^{-3t} \int 10 \cdot e^{3t} dt + K e^{-3t}$$

$$i(t) = 10e^{-3t} \cdot \frac{e^{3t}}{3} + K e^{-3t}$$

$$i(t) = \frac{10}{3} + K e^{-3t} \quad \text{--- (1)}$$

Initially
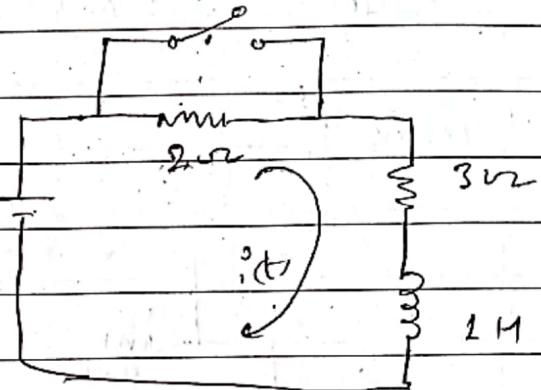
$$\begin{aligned} i(0) &= \frac{10}{3+2} \\ &= 2 \end{aligned}$$




for (1)

~~$i(0) = \frac{10}{3} + K e^{-3 \cdot 0}$~~

~~$K = -\frac{4}{3}$  from (1)  $i(t) = \frac{10}{3} - \frac{4}{3} e^{-3t}$  Res.  $\underline{\underline{=}}$~~

(b) Final Ckt.

Applying: KVL or mesh analysis

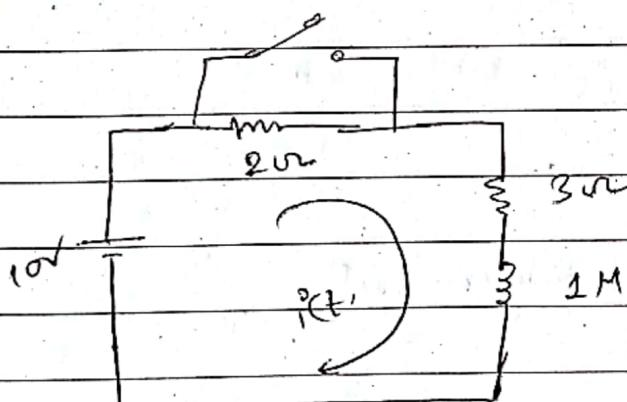

$$-2i(t) - 3i(t) - 1 \cdot \frac{di(t)}{dt} + 10 = 0$$

$$5i(t) + 1 \cdot \frac{di(t)}{dt} = 10$$

$$\frac{di(t)}{dt} + 5i(t) = 10$$

$$\text{Ans - } p = 5 \text{ and } Q = 10$$

then


$$i(t) = e^{-5t} \int 10e^{5t} dt + ke^{-5t}$$

$$i(t) = 10e^{-5t} \cdot \frac{e^{5t}}{5} + ke^{-5t}$$

$$i(t) = 2 + ke^{-5t} \quad (\text{year so})$$

initially,

$$i(0) = 2 + k = \frac{10}{3}$$

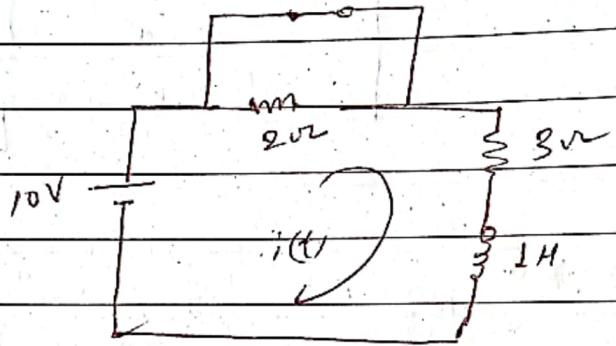

and  $\circledcirc$  at  $t=0^-$


$$\cancel{2} \cdot \frac{10}{3} = 2 + k \cancel{e^0}$$

$$\frac{4}{3} = k$$

thus,
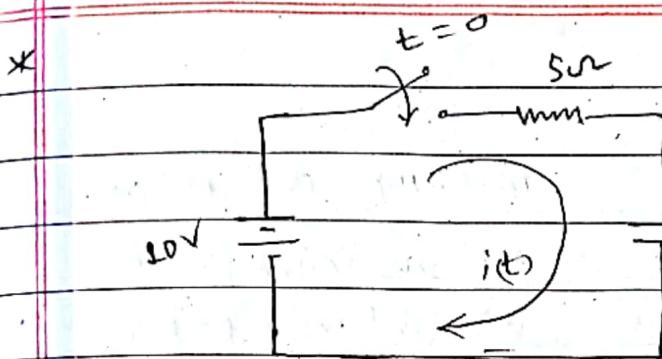
$$i(t) = 2 + \frac{4}{3} e^{-5t} \quad \text{particular soln.}$$






\* Switch is closed at

$t = 0$ . Find the current response.

Final circ.

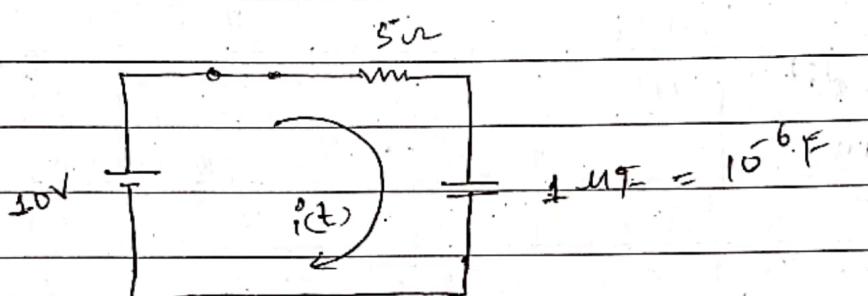

Applying mesh analysis:-

$$-5i(t) - \frac{1}{10^6} \int i(t) dt + 10 = 0$$

$$\text{or}, \quad 5i(t) + 10^6 \int i(t) dt = 10 \quad \text{--- (1)}$$

Differentiating both sides w.r.t. t.

$$5 \cdot \frac{d i(t)}{dt} + 10^6 i(t) = 0$$


$$\frac{d i(t)}{dt} + \frac{10^6}{5} i(t) = 0$$

$$\frac{d i(t)}{dt} = -\frac{10^6}{5} i(t)$$

Integrating.

$$i(t) = K e^{-\frac{10^6}{5} t} \quad \text{--- (2)}$$

Initially,

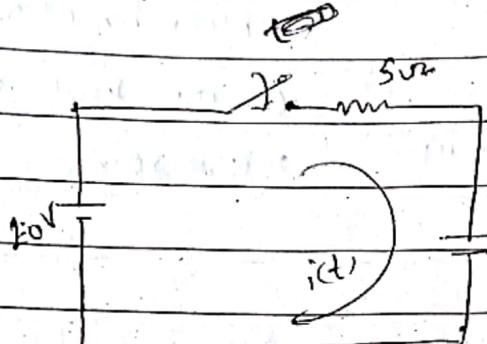

initially switch is open

so no charge is stored in capacitor  
i.e.  $V(0^-) = 0$

for Q①

$$5i(t) + \text{_____} = 10$$

$$i(t) = 2$$

$$i(t) = 2 \text{ Amp}$$

from ②  $2 = kC$

At  $t = 0^-$   $k = 2$ .


Now in ①  $R_3$  is 0.

$$-\frac{10^6}{5}t$$

$$\Rightarrow i(t) = 2e^{-\frac{10^6}{5}t}$$

R
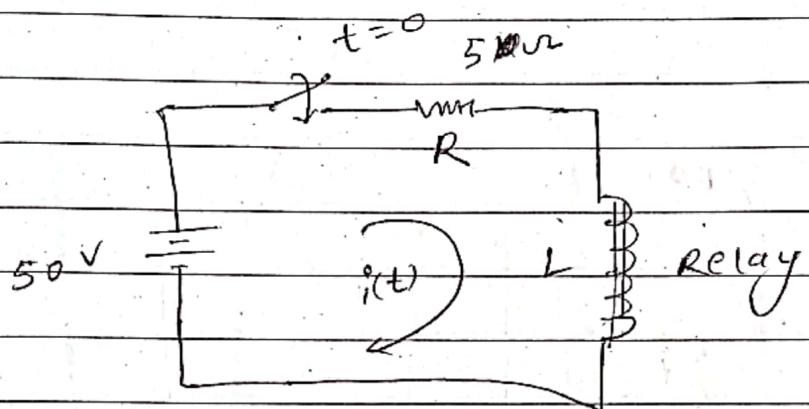
# In the given circuit, the relay is adjusted to operate with a current of 7 mA. Switch is closed at  $t=0$ . It is found the relay operates at  $t=0.2$  sec. Find (i) inductance  $L$  of the relay coil  
(ii) equation of the current  $i(t)$



Sol At  $t=0$ , switch is closed. Applying KVL

$$5i(t) + L \frac{di(t)}{dt} = 50$$

$$\text{or, } L \frac{di(t)}{dt} + 5i(t) = 50$$

$$\text{or, } \frac{di(t)}{dt} + \frac{5}{L} i(t) = \frac{50}{L}$$

$$\rho = \frac{5}{L}, \quad Q = \frac{50}{L}$$

$$i(t) = e^{-\rho t} \int Q \cdot e^{\rho t} dt + k e^{-\rho t}$$

$$\text{or, } i(t) = e^{-\frac{5}{L}t} \int \frac{50}{L} \cdot e^{\frac{5}{L}t} dt + k e^{-\frac{5}{L}t}$$

$$i^o(t) = \frac{50}{L} e^{-\frac{5}{L}t} \cdot \frac{e^{\frac{5}{L}t}}{\frac{5}{L}} + K e^{-\frac{5}{L}t}$$

$$i^o(t) = 10 + K e^{-\frac{5}{L}t}$$

general solution:

$$\text{Initially } i^o(0^-) = 0$$

put in general sol?

$$0 = 10 + K e^{-\frac{5}{L} \times 0}$$

$$K = -10$$

$$\Rightarrow i^o(t) = 10 - 10 e^{-\frac{5}{L} t}$$

$$\text{At } t = 0.2 \text{ sec, } i^o(t) = 7 \text{ mA}$$

$$7 \times 10^{-3} = 10 - 10 e^{-\frac{5}{L} \times 0.2} \quad \text{Eq^n of current}$$

$$7 \times 10^{-3} = 10 - 10 e^{-\frac{1}{L}}$$

$$i(t) = 10 - 10 e^{-\frac{5}{L} t}$$

$$= 3.5 \times 10^{-3} t$$

$$\Rightarrow i(t) = 10 - 10 e^{-\frac{5}{L} t}$$


$$e^{-\frac{1}{L}} = 0.9993$$

$$-\frac{1}{L} = -7 \times 10^{-3}$$

$$L = 1428.07 \text{ H}$$

## # Parallel circuit.

①

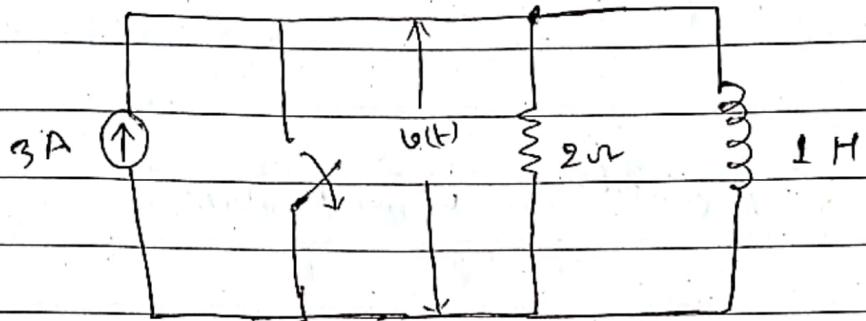


switch is opened at  $t = 0$ .

Find the voltage response  $v(t)$ . Also find current through inductor.

Sol At  $t = 0$ , switch is opened.

Applying KCL,

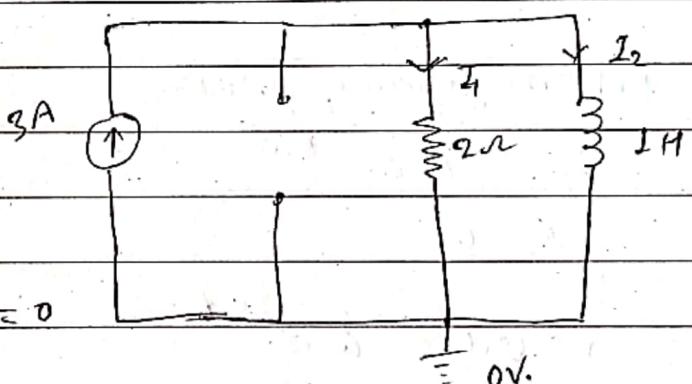

$$3 - I_1 - I_2 = 0$$

$$\text{in } 3 - \frac{v(t)}{2} - \frac{1}{L} \int v(t) dt = 0$$

$$\text{or, } \frac{v(t)}{2} + \frac{1}{L} \int v(t) dt = 3 \quad \text{--- (1)}$$

Differentiating above equation

$$\frac{1}{2} \frac{d v(t)}{dt} + \frac{1}{L} v(t) = 0$$

$$\frac{d v(t)}{dt} + 2 L v(t) = 0$$

$$\text{I} \frac{dV(t)}{dt} = -2V(t)$$

$$\text{or } \frac{dV(t)}{V(t)} = -2dt$$

Integrating


$$V(t) = Ke^{-2t} \quad \text{--- general solution}$$

Initially,  $t=0^-$

From ①

$$\frac{V(0)}{2} + 0 = 3$$

$$V(0^-) = 6$$

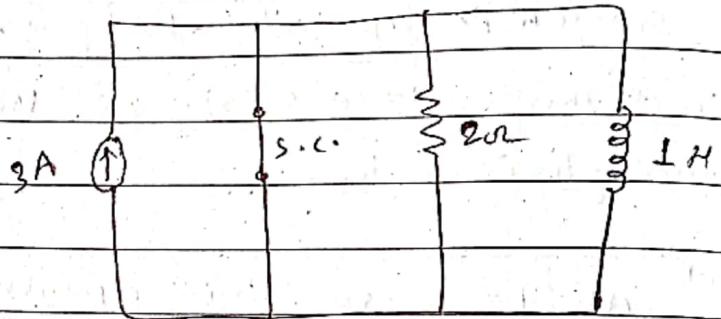

put in general solution,

$$6 = Ke^{-2t}$$

$$K = 6$$

$$\Rightarrow V(t) = 6e^{-2t}$$


$$\text{current through inductor } i_2(t) = \frac{1}{L} \int V(t) dt$$

$$= \frac{1}{1} \int 6e^{-2t} dt$$

$$= \frac{6e^{-2t}}{-2} + C$$

$$i_2(t) = -3e^{-2t} + C$$

Q

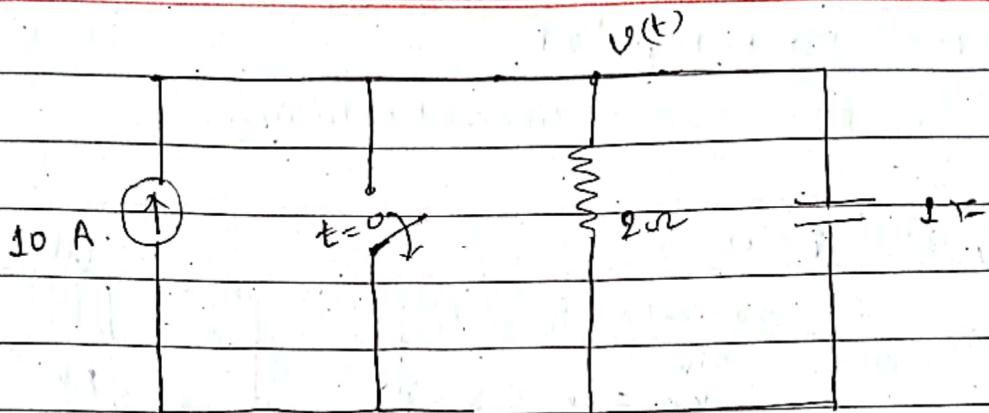


switch is opened at  $t = 0$ .

Find the voltage response  $v(t)$  and current through capacitor.

so,

At  $t = 0$ , switch is opened.

Applying KCL,

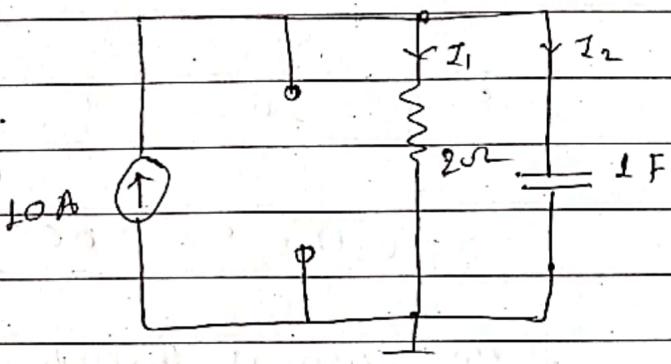

$$I_0 = I_1 + I_2$$

$$\text{or } I_0 = \frac{v(t)}{2} + C \cdot \frac{dv(t)}{dt}$$

$$\text{or, } \frac{d v(t)}{dt} + \frac{v(t)}{2} = I_0$$

If initially voltage  
at  $t=0$  was not initial  
and if we use it

$$P = \frac{1}{2}, Q = 10$$

$$\text{then } v(t) = e^{-Pt} \int Q \cdot e^{Qt} dt + k e^{-Pt}$$

$$v(t) = e^{-\frac{1}{2}t} \int 10 \cdot e^{\frac{1}{2}t} dt + k e^{-\frac{1}{2}t}$$

$$= e^{-\frac{1}{2}t} \cdot \frac{10 \cdot e^{\frac{1}{2}t}}{\frac{1}{2}} + k e^{-\frac{1}{2}t}$$

$$\text{or } V(t) = 20 + K e^{-1/2 t}$$

general solution.

Initially at  $t = 0^-$

$$V(0^-) = 0 \text{ V.} \quad \begin{array}{l} (\text{Initial } 5\text{V first}) \\ \text{at } t=0^- \\ V(0^-) = 5\text{V} \\ \frac{dV}{dt}(0^-) \end{array}$$

Then from general  
solution,

$$0 = 20 + K e^{-1/2 \times 0}$$

same.

$$\therefore K = -20$$

$$\Rightarrow V(t) = 20 - 20 e^{-1/2 t}$$

Now current through capacitor


Capacitor FT voltage,  
 $V_{FT} = \frac{1}{2} \text{ initial voltage } \times t$

$$i_c(t) = C \frac{dV_{FT}}{dt}$$


$$= C \frac{d}{dt} (20 - 20 e^{-1/2 t})$$

$$= -20 \times e^{-1/2 t} \times -\frac{1}{2}$$

$$= 10 e^{-1/2 t}$$

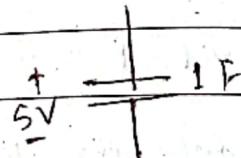

(3)

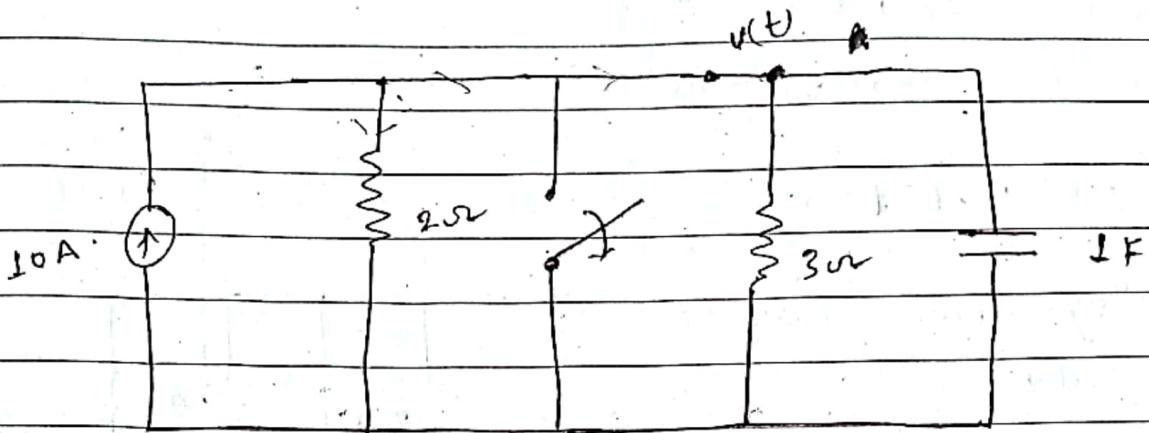

switch is opened at  $t = 0$

find  $u(t)$  at  $t \geq 0$ .

$\Rightarrow$  At  $t = 0$ , switch is opened.

applying KCL

$$10 = I_1 + I_2 + I_3$$

$$\text{or}, \frac{u(t)}{2} + \frac{u(t)}{3} + L \cdot \frac{d u(t)}{dt} = 10$$

$$\text{or}, \frac{5}{6} u(t) + \frac{d u(t)}{dt} = 10$$

$$\text{or}, \frac{d u(t)}{dt} + \frac{5}{6} u(t) = 10$$


which is non-homogeneous linear diff - eq.

$$P = \frac{5}{6}, Q = 10$$

$$u(t) = e^{-Pt} \int Q \cdot e^{Pt} dt + K e^{-Pt}$$

$$= e^{-\frac{5}{6}t} \int 10 e^{\frac{5}{6}t} dt + K e^{-\frac{5}{6}t}$$
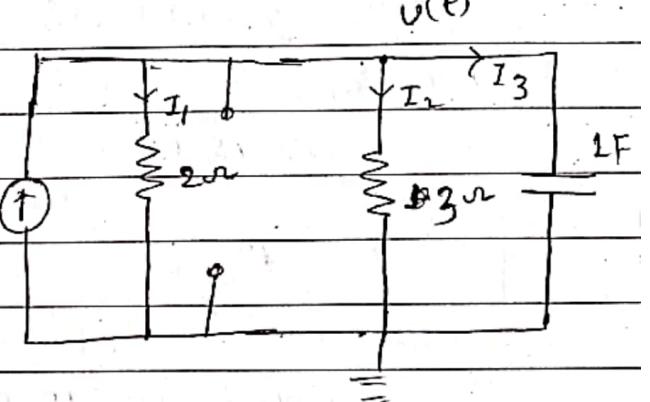
$$= e^{-\frac{5}{6}t} \cdot 10 \cdot e^{\frac{5}{6}t} \cdot \frac{6}{5} + K e^{-\frac{5}{6}t}$$




$$V(t) = 12 + k e^{-5/6 t}$$

which is general solution.

Initially at  $t=0^-$

voltage across capacitor  
= 0V
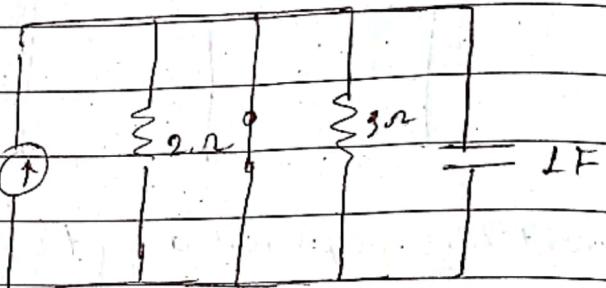
$$\text{No. } V(0^-) = V(0^+) = 0V. \quad 10A$$



Then, general sol?

becomes,

$$0 = 12 + k e^{-5/6 t^0}$$

$$k = -12$$


Then,

$$V(t) = 12 - 12 e^{-5/6 t}$$

Ans.

H.W

Date \_\_\_\_\_  
Page \_\_\_\_\_

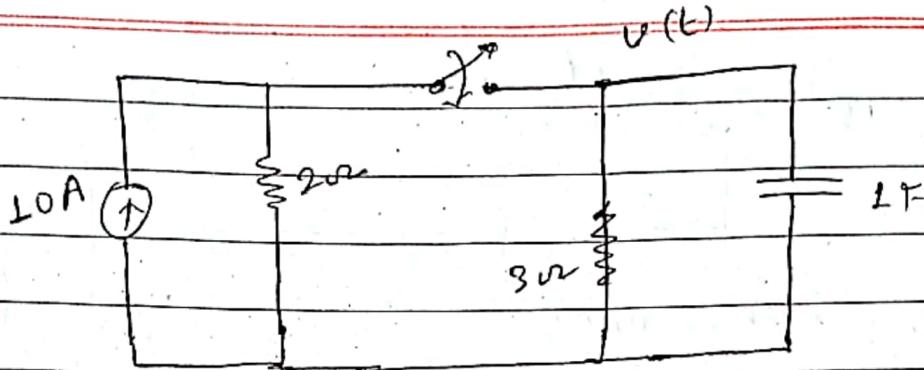

Switch is closed at  $t=0$ .

Find the voltage response  $v(t)$ .

At  $t=0$  switch is closed.

Applying KCL,

neg.

$$I_1 + I_2 + I_3 = 10$$

$$\text{or}, \frac{v(t)}{2} + \frac{v(t)}{3} + 1 \cdot \frac{d(v(t))}{dt} = 10$$

$$\text{or}, \frac{5}{6} v(t) + \frac{d(v(t))}{dt} = 10$$

$$\text{or}, \frac{d(v(t))}{dt} + \frac{5}{6} v(t) = 10$$


which is non homogeneous diff. eq?

$$\text{where } p = \frac{5}{6}, g = 10$$

$$v(t) = e^{\int g e^{pt} dt} + k e^{-pt}$$

$$= e^{-\frac{5}{6}t} \int 10 \cdot e^{\frac{5}{6}t} dt + k e^{-\frac{5}{6}t}$$
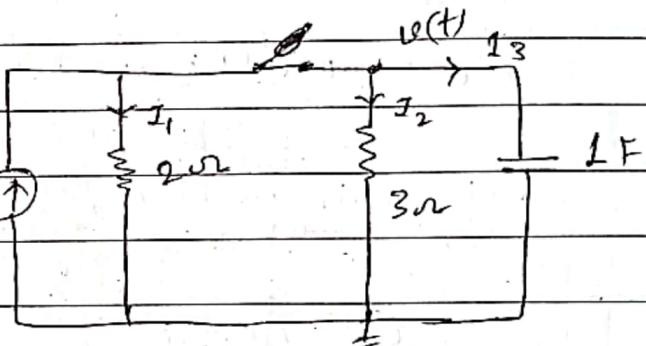
$$= e^{-\frac{5}{6}t} \cdot \frac{10 \cdot e^{\frac{5}{6}t}}{\frac{5}{6}} + k e^{-\frac{5}{6}t}$$



$$v(t) = 12 + k e^{-\frac{5}{16}t}$$


general sol?

At initially, switch is open,

At  $t = 0^-$ , voltage

across capacitor is  
20V.

$$v(0^-) = v(0^+) = 20$$

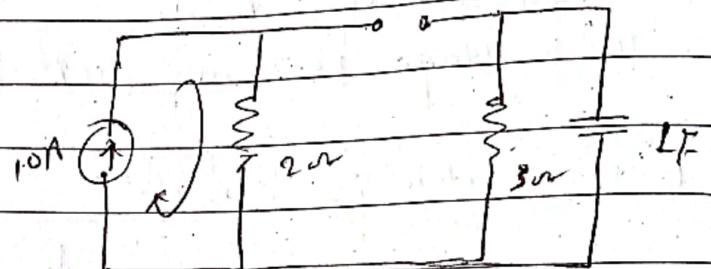

then from general sol

$$-\frac{5}{16} \times 0$$

$$0 = 12 + k e^{-\frac{5}{16} \times 0}$$

$$k = -12$$

$$-\frac{5}{16}t$$

$$\text{and, } v(t) = 12 - 12e^{-\frac{5}{16}t}$$

At  $t = 0^-$ , voltage drop across  $2\Omega \Rightarrow 2 \times 10 = 20V$

$$\therefore v(0^-) = v(0^+) = 20V$$


$$\text{then, } 20 = 12 + k e^{-\frac{5}{16} \times 0}$$

$$k = 8$$

$$-\frac{5}{16}t$$

$$\therefore v(t) = 12 + 8 e^{-\frac{5}{16}t}$$

## # Input as exponential function

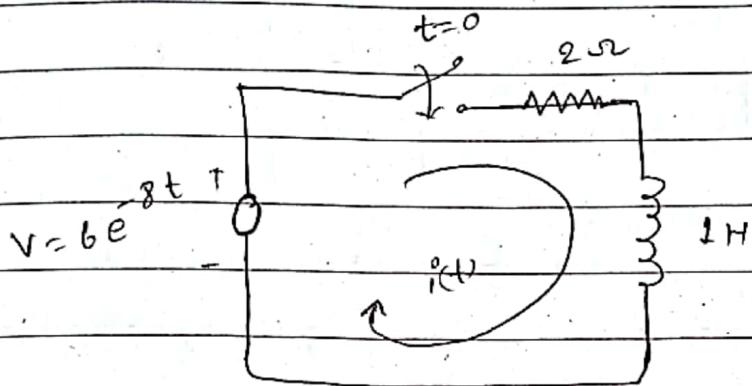

switch is closed at  $t=0$ . Find the current response.

OR,

A resistor of  $2\Omega$  and an inductor inductance  $1H$  in series are suddenly connected to a voltage source of  $6e^{-8t}$  at  $t=0$ . Find the current response. Assume no initial current through inductor.

Sol?

At  $t=0$ , using KVL

$$2i(t) + 1 \cdot \frac{di(t)}{dt} = 6e^{-8t}$$

$$\frac{di(t)}{dt} + 2i(t) = 6e^{-8t} \quad \text{--- non homogeneous.}$$

$$p = 2, \quad q = 6e^{-8t}$$

$$i(t) = e^{-pt} \int q \cdot e^{pt} dt + k e^{-pt}$$

$$= e^{-2t} \int 6e^{-8t} \cdot e^{2t} dt + k e^{-2t}$$

$$= e^{-2t} \cdot \frac{6 \cdot e^{-6t}}{-6} + k e^{-2t}$$

$i(t) = -e^{-8t} + k e^{-2t}$  - general solution.

Initial:  $i(0^-) = 0$

$$\therefore i(0^+) = i(0^-) = 0$$

Then,

$$0 = -e^{-8 \times 0} + k e^{-2 \times 0}$$


$$0 = -1 + k$$

$$k = 1$$

$$\therefore i(t) = -e^{-8t} + e^{-2t}$$

Ans.

Q.

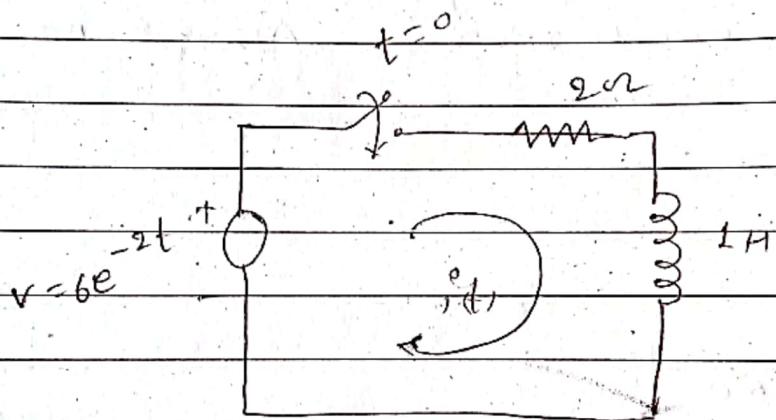

Switch is closed at  $t=0$

Find current response.

at  $t=0$ , using KVL

$$2i(t) + \frac{di(t)}{dt} = 6e^{-2t}$$

$$p = 2, q = 6e^{-2t}$$

$$i(t) = e^{-2t} \int 6 \cdot e^{2t} \cdot e^{2t} dt + k e^{-2t}$$

$$i(t) = 6t e^{-2t} + k e^{-2t}$$

Initially,  $i(0^-) = 0$


then,

$$0 = 6 \times 0 \times e^{-2 \times 0} + k e^{-2 \times 0}$$

$$k = 0$$

$$\text{The } i(t) = 6t e^{-2t}$$

Q # Input as sinusoidal function

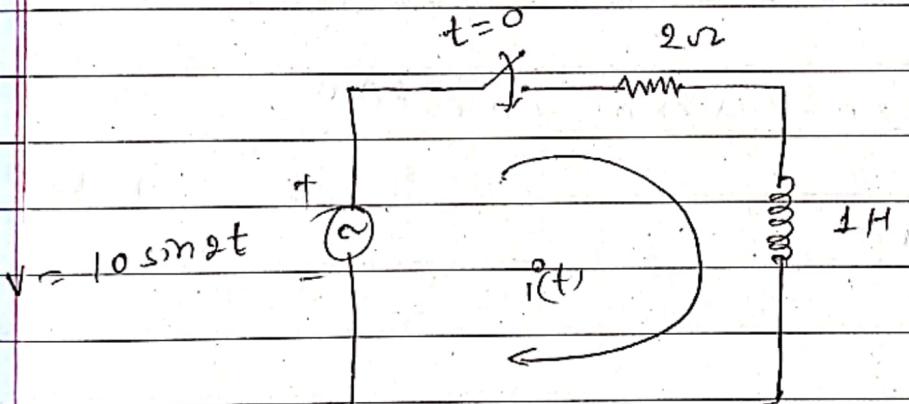

Switch is closed at  $t=0$ , Find the current response.

At  $t=0$ , applying KVL

$$2i(t) + 1 \cdot \frac{di(t)}{dt} = 10\sin 2t$$

$$\frac{di(t)}{dt} + 2i(t) = 10\sin 2t$$

non-homogeneous diff eq with  $p = 2$  and  $q = 10\sin 2t$

$$\int e^{\alpha x} \sin bx dx = \frac{e^{\alpha x}}{\alpha^2 + b^2} (\alpha \sin bx - b \cos bx)$$

Date \_\_\_\_\_  
Page \_\_\_\_\_

Ques.

$$\begin{aligned}
 i(t) &= e^{-pt} \int \phi e^{pt} dt + k e^{-pt} \\
 &= e^{-2t} \int 10 \sin 2t e^{2t} dt + k e^{-2t} \\
 &= 10 e^{-2t} \int e^{2t} \sin 2t dt + k e^{-2t} \\
 &= 10 e^{-2t} \cdot \frac{e^{2t}}{4+4} (2 \sin 2t - 2 \cos 2t) + k e^{-2t} \\
 &= \frac{5}{2} (2 \sin 2t - 2 \cos 2t) + k e^{-2t} \\
 &= \frac{5}{2} (\sin 2t - \cos 2t) + k e^{-2t}.
 \end{aligned}$$

Initially,

$$i(0^-) = 0$$

then,

$$0 = \frac{5}{2} (\sin 2 \times 0 - \cos 2 \times 0) + k e^{-2 \times 0}$$

$$0 = -\frac{5}{2} + k e^{-2 \times 0}$$

$$k = \frac{5}{2}$$

Thn,


$$i(t) = \frac{5}{2} (\sin 2t - \cos 2t) + \frac{5}{2} e^{-2t}.$$

$$i(t) = \frac{5}{2} (\sin 2t - \cos 2t + e^{-2t})$$

Amp.

$$\int e^{on} \cos bndn = \frac{e^{on}}{a^2 + b^2} (\cos bn + b \sin bn)$$

Date \_\_\_\_\_  
Page \_\_\_\_\_

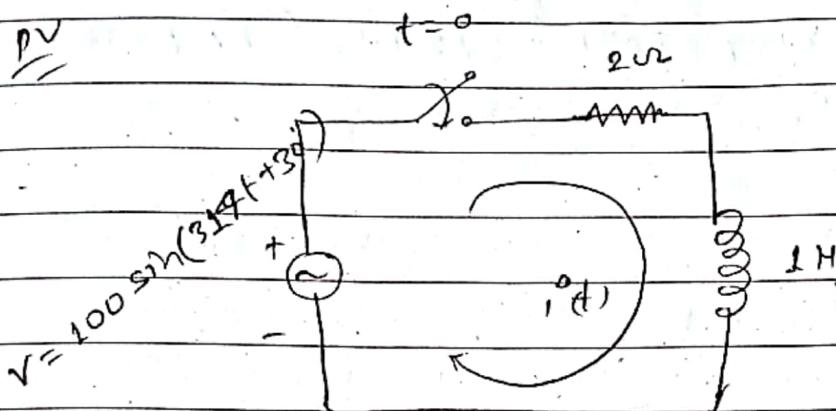

switch is closed at  $t = 0$ , Find the current response.

$\text{At } t = 0 \text{ second, applying KVL.}$

$$2i(t) + 1 \cdot \frac{di(t)}{dt} = 100 \sin(314t + 30^\circ)$$

which is non homogeneous diff eq. with

$$P = 2, Q = 100 \sin(314t + 30^\circ)$$

ans.

$$i(t) = e^{-2t} \int 100 \sin(314t + 30^\circ) \cdot e^{2t} dt + k e^{-2t}$$

$$= 100 e^{-2t} \int e^{2t} \sin(314t + 30^\circ) dt + k e^{-2t}$$

$$= 100 e^{-2t} \cdot \frac{e^{2t}}{4 + 314^2} [2 \sin(314t + 30^\circ) - 314 \cos(314t + 30^\circ)] + k e^{-2t}$$

$$= \frac{100}{98600} [2 \sin(314t + 30^\circ) - 314 \cos(314t + 30^\circ)]$$

$$+ k e^{-2t}$$

$$i(t) = \frac{1}{986} \left\{ 2 \sin(314t + 30^\circ) - 819 \cos(314t + 30^\circ) \right\} + ke^{-2t}$$

Initially,  $i^o(0^-) = 0$ ,

then general  $i(t)$  becomes,


$$\frac{1}{986} \left\{ 2 \sin(0 + 30^\circ) - 819 \cos(0 + 30^\circ) \right\} + ke^{-2 \times 0} =$$

$$\approx -0.275 + ke^0 = 0$$

$$k = 0.275$$

thus
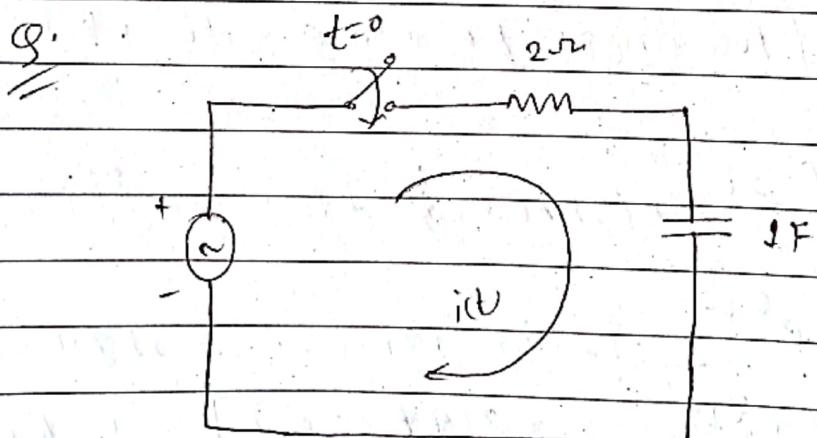
$$i(t) = \frac{1}{986} \left\{ 2 \sin(314t + 30^\circ) - 819 \cos(314t + 30^\circ) \right\} + 0.275 e^{-2t}$$



$$V = 100 \sin(314t + 30^\circ)$$

Switch is closed at  $t=0$ , Find the current response.

At  $t = 0$ , circuit is closed then using LPRZ,

$$2 i(0) + \frac{1}{L} \cdot \int i(t) dt = 100 \sin(314t + 30^\circ)$$

Differentiating w.r.t. t.

$$2 \frac{d i(t)}{dt} + i(0) = 100 \cos(314t + 30^\circ) \times 314$$

$$n, \frac{d i(t)}{dt} + \frac{1}{2} i(0) = 31400 \cos(314t + 30^\circ)$$

Non homogeneous diff. eq. with

$$P = \frac{1}{2}, Q = 31400 \cos(314t + 30^\circ)$$

then

$$i(t) = e^{-\frac{1}{2}t} \int 31400 \cos(314t + 30^\circ) \cdot e^{\frac{1}{2}t} dt + k e^{-\frac{1}{2}t}$$

$$= 31400 \cancel{e^{-\frac{1}{2}t}} \cdot \cancel{\frac{e^{\frac{1}{2}t}}{\frac{1}{4} + 314^2}} \left[ \frac{1}{2} \cos(314t + 30^\circ) + 314 \sin(314t + 30^\circ) \right] + k e^{-\frac{1}{2}t}$$

$$i(t) = \frac{0.381}{0.3185} \left( \frac{1}{2} \cos(314t + 30^\circ) + 314 \sin(314t + 30^\circ) \right) + k e^{-\frac{1}{2}t}$$

Since, initially switch is open so voltage across capacitor is 0V.

$$\text{also } V(0^-) = V(0^+)$$

so from ①

$$2 i(t) + 0 = 100 \sin(314t + 30^\circ)$$

$$i(t) = 50 \sin(\cancel{314} + 30^\circ) = 25$$

from (2)

$$50 \sin(314t + 30^\circ) =$$

$$25 = 0.3185 \left\{ \frac{1}{2} \cos 30^\circ + 314 \sin 30^\circ \right\} + K$$


$$\Rightarrow K = -78.9 \times$$

Again from (2)

$$i(t) = 0.3185 \left\{ \frac{1}{2} \cos(314t + 30^\circ) + 314 \sin(314t + 30^\circ) \right\} - 78.9 \times e^{-\frac{1}{2}t}$$


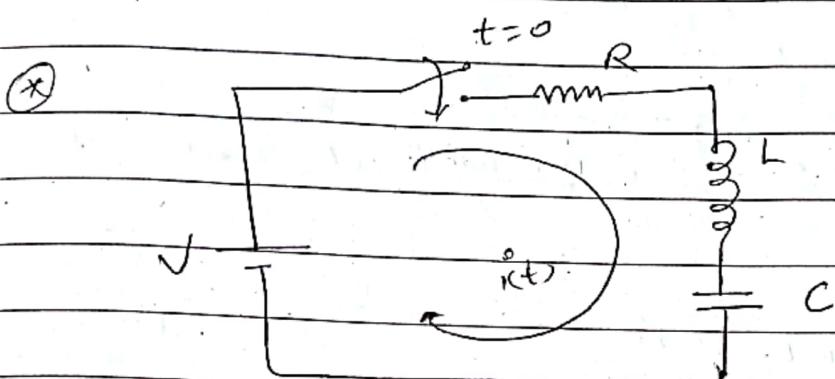
# step function response of RLC series circuit;



switch is closed at  $t = 0$ , find the current response.

Sol: At  $t = 0$  switch is closed. applying KVL

$$-Ri(t) - L \frac{di(t)}{dt} - \frac{1}{C} \int i(t) dt + v = 0$$

$$\text{or, } L \frac{di(t)}{dt} + Ri(t) + \frac{1}{C} \int i(t) dt = v \quad \dots \textcircled{1}$$

Differentiating above eq<sup>1</sup>.

$$L \frac{d^2 i(t)}{dt^2} + R \frac{di(t)}{dt} + \frac{1}{C} i(t) = 0$$

$$\frac{d^2 i(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{1}{LC} i(t) = 0$$

characteristics eq<sup>2</sup>,

$$m^2 + \frac{R}{L} m + \frac{1}{LC} = 0$$

Let,  $m_1$  and  $m_2$  be solution or roots of the given eq<sup>2</sup>.

then,

$$-b \pm \sqrt{b^2 - 4ac}$$

$$m_1, m_2 = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$\text{or } m_1, m_2 = -\frac{R}{L} \pm \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}}$$

Case I: when  $\frac{4}{LC} < \frac{R^2}{L^2}$ , we will get real and distinct roots.

say  $m_1$  and  $m_2$ .

$$\Rightarrow i(t) = k_1 e^{m_1 t} + k_2 e^{m_2 t}$$


Case II: when  $\frac{4}{LC} = \frac{R^2}{L^2}$ , we will get real and equal root say

$$m_1 = m_2 = m.$$

$$\Rightarrow i(t) = (k_1 + k_2 t) e^{mt}$$

Case III: when  $\frac{4}{LC} > \frac{R^2}{L^2}$ , we will get imaginary roots say  $m_1 \pm jm_2$ .
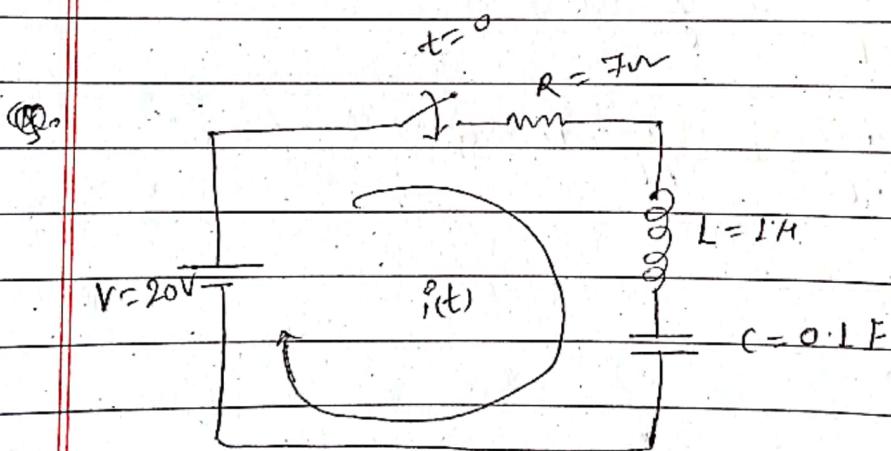
$$\Rightarrow i(t) = e^{mt} (k_1 \cos m_2 t + k_2 \sin m_2 t)$$



switch is closed at  $t = 0$ .

Find the complete solution for current.

5) At  $t = 0$ , switch is closed.

applying KVL

$$-7i(t) - 1 \cdot \frac{di(t)}{dt} - \frac{1}{0.1} \int i(t) dt + 20 = 0$$

$$\text{or, } \frac{di(t)}{dt} + 7i(t) + 10 \int i(t) dt = 20 \quad \text{--- (1)}$$

Dif. w.r.t. to  $t$ .

$$\frac{d^2 i(t)}{dt^2} + 7 \frac{di(t)}{dt} + 10 i(t) = 0$$

characteristics eq?

$$m^2 + 7m + 10 = 0$$

$$(m+5)(m+2) = 0$$

$$m = -2, -5$$

$$\Rightarrow i(t) = k_1 e^{-2t} + k_2 e^{-5t}$$

It is general equation.

Now, Initial current  $i(0^-) = 0$

$$\text{then, } 0 = k_1 e^{-2 \times 0} + k_2 \times e^{-5 \times 0}$$

$$k_1 + k_2 = 0 \quad \text{--- (2)}$$

Dif. general eq?

$$\frac{di(t)}{dt} = -2k_1 e^{-2t} + 5k_2 e^{-5t}$$

from (1) using initial condition i.e.  $v(0^-) = 0$  across capacitor we get,

$$\frac{di(t)}{dt} + 7 \times 0 + 0 = 20$$

$$\frac{di(t)}{dt} = 20$$

Then,

$$20 = -2k_1 e^{-2t} - 5k_2 e^{-5t}$$

$$\text{or}, -2k_1 - 5k_2 = 20 \quad \text{--- (3)}$$

Solving (2) and (3) we get


$$k_1 = 20/3$$

$$k_2 = -20/3$$

Then general soln becomes

$$i(t) = \frac{20}{3} e^{-2t} - \frac{20}{3} e^{-5t} \quad \text{which is complete soln.}$$

Q.

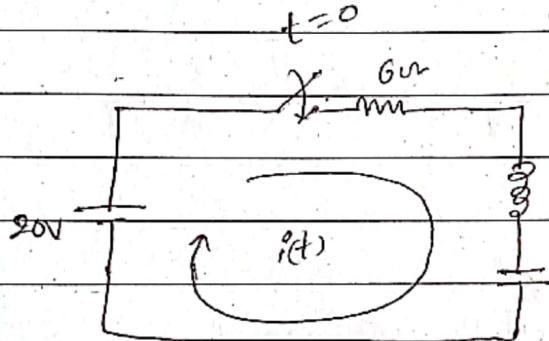Switch is closed at  $t=0$ 

Find complete soln for current?

At  $t=0$ , switch is closed.

Applying KVL,

$$-6i(t) - 1 \cdot \frac{di(t)}{dt} - 9 \int i(t) dt + 20 = 0$$

$$\text{or}, \frac{d^2i(t)}{dt^2} + 6 \frac{di(t)}{dt} + 9 \int i(t) dt = 20 \quad \text{--- (1)}$$

Diff (1) w.r.t t.

$$\frac{d^2i(t)}{dt^2} + 6 \frac{di(t)}{dt} + 9i(t) = 0$$

characteristics eqn

$$m^2 + 6m + 9 = 0$$

$$(m+3)(m+3) = 0$$

$$m = -3, -3.$$

Then the general soln is

$$\Rightarrow i(t) = (k_1 + k_2 t) e^{-3t}$$

Initially,  $i(0) = 0$

$$\text{So, } 0 = (k_1 + k_2 \times 0) e^{-3t}$$

$$k_1 = 0$$

∴

$$\Rightarrow i(t) = k_2 t e^{-3t}$$

diff. w.r.t t

$$\frac{d i(t)}{dt} = -3e^{-3t} \cdot k_2 t + k_2 e^{-3t}$$

Initially from Q1


$$\frac{d i(t)}{dt} + 6 \times 0 + 0 = 20$$

$$\text{then, } 20 = -3e^{-3 \times 0} \times k_2 \times 0 + k_2 \times e^{-3 \times 0}$$

$$k_2 = 20$$

Hence the complete solution is

$$\Rightarrow i(t) = 20t e^{-3t}$$

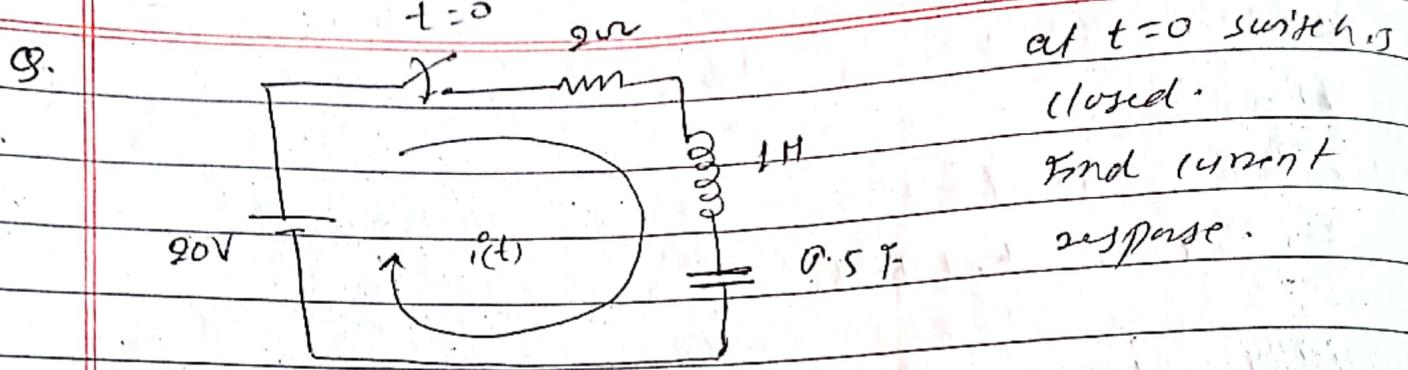

At  $t = 0$ , switch is closed.

Then applying KVL.

$$1. \frac{d^2 i(t)}{dt^2} + 2 \frac{di(t)}{dt} + \frac{1}{0.5} \int i(t) dt = 20 \quad \text{--- (1)}$$

Differentiating (1) w.r.t. to t.

$$\frac{d^2 i(t)}{dt^2} + 2 \frac{di(t)}{dt} + 2 i(t) = 0$$

Its characteristics eq'

$$m^2 + 2m + 2 = 0$$

$$m_1, m_2 = \frac{-2 \pm \sqrt{4 - 8}}{2}$$

$$= -1 \pm j1$$

Thus general sol is

$$\Rightarrow i(t) = e^{-t} (k_1 \cos t + k_2 \sin t)$$

Initially,  $i(0^-) = 0$

and voltage across capacitor  $v(0^-) = 0$

$$\text{then } e^{-0} (k_1 \times \cos 0 + k_2 \times \sin 0) = 0 \\ k_1 = 0$$

$$\Rightarrow \dot{i}(t) = e^{-t} \cdot k_2 \sin t$$

Diff. w.r.t. to t

$$\frac{d\dot{i}(t)}{dt} = -e^{-t} k_2 \sin t + e^{-t} k_2 \cos t$$

from ① initially

$$\frac{d\dot{i}(t)}{dt} + 2x_0 + 0 = 20$$

$$\text{Th, } 20 = -e^{-0} k_2 \times \sin 0 + e^{-0} k_2 \cos 0$$

$$k_2 = 20$$

then reqd eq is.

$$\Rightarrow \dot{i}(t) = 20 e^{-t} \sin t$$

\* For Non-homogeneous second order equation.

$$\text{complete solution: } i(t) = i_c(t) + i_p(t)$$

where,

$i_c(t)$  = complementary function obtained from the characteristics eq.

$i_p(t)$  = particular integral obtained from hit trial method by considering the forcing function.

For particular integral.

Forcing fun<sup>n</sup> / Input

Assumption of Particular Integral

(1) constant r

(1) constant k


(2)  $r e^{mt}$

(2)  $k e^{mt}$

(3)  $\cos \omega t + \sin \omega t$

(3)  $A \cos \omega t + B \sin \omega t$

Q.

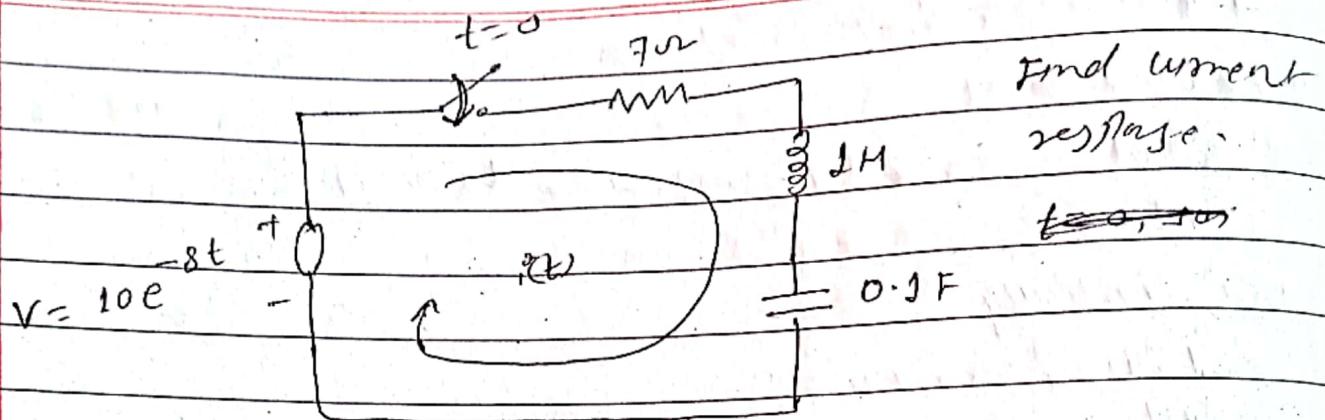

At  $t=0$ , switch is closed.

Applying KVL,

$$1 \cdot \frac{d^2 i(t)}{dt^2} + 7 i(t) + \frac{1}{0.1} \int i(t) dt = 10 e^{-8t} \quad \textcircled{1}$$

Diffr. ① w.r.t.  $t$

$$\frac{d^2 i(t)}{dt^2} + 7 \frac{d i(t)}{dt} + 10 i(t) = -80 e^{-8t} \quad \textcircled{2}$$

Its characteristic eqn

$$m^2 + 7m + 10 = 0$$

$$(m+5)(m+2) = 0$$

$$m = -2, m = -5$$

Then its complementary function

$$i_c(t) = k_1 e^{-2t} + k_2 e^{-5t} \quad \textcircled{3}$$

For particular integral,  $g = -80 e^{-8t}$

So,

$$i_p(t) = k_3 e^{-8t}$$

Diffr. w.r.t.  $t$ .

$$i_p'(t) = -8k_3 e^{-8t}$$

$$i_p''(t) = 64k_3 e^{-8t}$$

From eq ②

$$64k_3 e^{-8t} + 7 \cdot (-8) k_3 e^{-8t} + 10 k_3 e^{-8t} = -80e^{-8t}$$

by comparing equivalent coefficient  
we get;

$$64k_3 - 56k_3 + 10k_3 = -80$$

$$\Rightarrow k_3 = -\frac{40}{9}$$

$$\Rightarrow i_p(t) = -\frac{40}{9} e^{-8t}$$

Hence the general sol?

$$i(t) = i_c(t) + i_p(t)$$

$$\Rightarrow i(t) = k_1 e^{-2t} + k_2 e^{-5t} - \frac{40}{9} e^{-8t}$$

Initially,  $i(0^-) = 0$ . Then

$$k_1 + k_2 = \frac{40}{9} \quad \text{--- } ④$$

Diff general sol?

$$\frac{d i(t)}{dt} = -2k_1 e^{-2t} - 5k_2 e^{-5t} + \frac{320}{9} e^{-8t}$$

Initially using eq ①

$$\frac{d i(t)}{dt} + 7 \times 0 + 0 = 10 e^{-8t} \Big|_{t=0} = 10$$

$$\text{So, } 10 = -2k_1 e^{-2 \times 0} - 5k_2 e^{-5 \times 0} + \frac{320}{9} e^{-8 \times 0}$$

$$\textcircled{1} -2k_1 - 5k_2 + \frac{320}{9} = 10$$


$$-2k_1 - 5k_2 = -\frac{230}{9} \quad \text{--- } ⑤$$

Solving ④ &amp; ⑤

$$k_1 = -\frac{10}{9} \quad k_2 = \frac{50}{9}$$

$$\Rightarrow i(t) = -\frac{10}{9} e^{-2t} + \frac{50}{9} e^{-5t} - \frac{40}{9} e^{-8t}$$

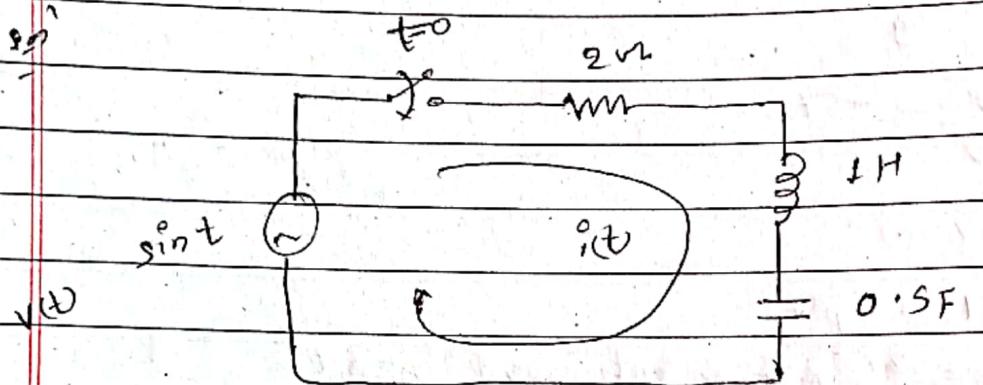- Q. A series RLC circuit with  $R = 2\Omega$ ,  $C = 0.5 F$  and  $L = 1 H$  is excited by a voltage of  $v(t) = \sin t$  for  $t \geq 0$ . For the elements values specified, find the current  $i(t)$  through the circuit if the switch is closed at  $t=0$ .



At  $t=0$ , the switch is closed.

Using KVL

$$1 \cdot \frac{di(t)}{dt} + \frac{1}{0.5} \int i(t) dt + 2i(t) = \sin t \quad \text{--- (1)}$$

After:

$$\frac{d^2 i(t)}{dt^2} + \frac{2}{0.5} \frac{di(t)}{dt} + 2i(t) = \cos t \quad \text{--- (2)}$$

which is non-homogeneous. So

characteristics eq is

$$m^2 + 2m + 2 = 0$$

$$m_1, m_2 = \frac{-2 \pm \sqrt{4 - 8}}{2}$$

$$m_1, m_2 = -1 \pm j1$$

$$\text{Then } i_p(t) = e^{-t} (k_1 \cos t + k_2 \sin t) \quad \text{--- (3)}$$

for  $i_p(t)$

$$i_p(t) = \cos(t)$$

$$i_p(t) = -\sin(t)$$

$$i_p(t) = -\cos t$$

from (2)

forcing function  $e^{-t}$  for  $i_p(t)$

$$-\cos t$$

for  $i_p(t)$

$$i_p(t) = k_3 \cos t + k_4 \sin t$$

$$i_p(t) = -k_3 \sin t + k_4 \cos t$$

$$i_p(t) = -k_3 \cos t - k_4 \sin t$$

from (2)

$$-k_3 \cos t - k_4 \sin t - 2k_3 \sin t + 2k_4 \cos t + 2k_3 \cos t +$$

$$2k_4 \sin t = \cos t$$

$$\text{or } (-k_3 + 2k_4 + 2k_3) \cos t + (-k_4 - 2k_3 + 2k_4) \sin t = \cos t$$

equating like terms,

$$k_3 + 2k_4 = 1$$

$$-2k_3 + k_4 = 0$$

$$\text{Solving, } k_3 = \frac{1}{5}, k_4 = \frac{2}{5}$$

$$i_p(t) = \frac{1}{5} \cos t + \frac{2}{5} \sin t \quad \text{--- (4)}$$

No. 2 general solution is

$$\overset{\circ}{i}(t) = \overset{\circ}{i}_c(t) + i_p(t)$$

$$\overset{\circ}{i}(t) = e^{-t} (\kappa_1 \cos t + \kappa_2 \sin t) + \frac{1}{5} \cos t + \frac{2}{5} \sin t$$

Initially,  $\overset{\circ}{i}(0^-) = 0$  mma,

$$0 = (\kappa_1 + 0) + \frac{1}{5}$$

$$\kappa_1 = -\frac{1}{5}$$

Dif. gen. soln:

$$\begin{aligned} \frac{d \overset{\circ}{i}(t)}{dt} &= -e^{-t} (\kappa_1 \cos t + \kappa_2 \sin t) + e^{-t} (-\kappa_1 \sin t + \kappa_2 \cos t) \\ &\Rightarrow \frac{1}{5} \sin t + \frac{2}{5} \cos t \end{aligned}$$

Initially, from (i)

$$\frac{d \overset{\circ}{i}(t)}{dt} + 0 + 0 = \sin 0$$

$$\frac{d \overset{\circ}{i}(t)}{dt} = 0$$

then


$$0 = -1 \cdot \left(-\frac{1}{5}\right) + 1 \cdot (\kappa_2) - 0 + \frac{2}{5}$$

$$0 = \frac{1}{5} + \frac{2}{5} + \kappa_2$$

$$\kappa_2 = -\frac{3}{5}$$

$$\text{Hence, } \overset{\circ}{i}(t) = e^{-t} \left( -\frac{1}{5} \cos t + \frac{3}{5} \sin t \right) + \frac{1}{5} \cos t + \frac{2}{5} \sin t$$

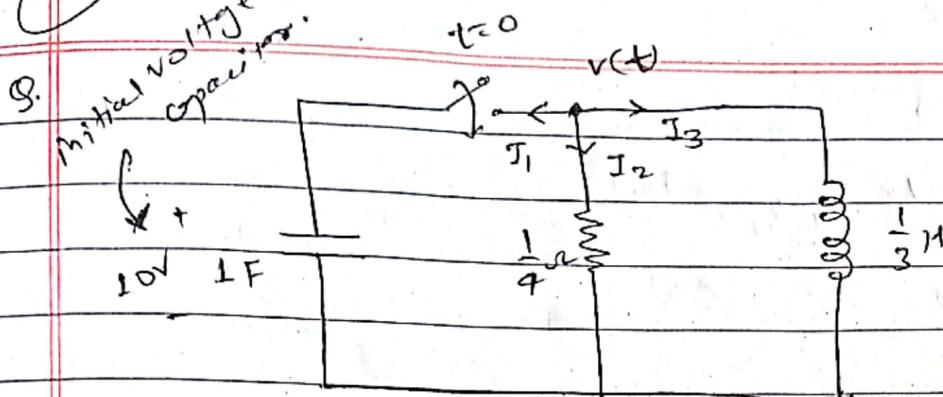P.V.  
Initial voltage across  
capacitor.



Switch is closed at  $t = 0$ .

Find the voltage and current through inductor.

At  $t = 0$ , Applying KCL:

$$I_1 + I_2 + I_3 = 0$$

$$C \frac{dV(t)}{dt} + \frac{V(t)}{R} + \frac{1}{L} \int V(t) dt = 0$$

$$1. \frac{dV(t)}{dt} + 4V(t) + 3 \int V(t) dt = 0 \quad \text{--- (1)}$$

Diff. w.r.t to  $V(t)$

$$\frac{d^2V(t)}{dt^2} + 4 \frac{dV(t)}{dt} + 3V(t) = 0$$

Homogeneous eq?

Its characteristic eq?

$$m^2 + 4m + 3 = 0$$

Solving

$$m = -1, -3$$

$$V(t) = k_1 e^{-1-t} + k_2 e^{-3t} \quad \text{--- general solution.}$$

Since  $V(0) = 10$

so,

$$10 = k_1 e^{-2t} + k_2 e^{-3t}$$

$$k_1 + k_2 = 10 \quad \text{--- (2)}$$

Dif. eqn. so?

$$\frac{dV(t)}{dt} = -k_1 e^{-t} - 3k_2 e^{-3t}$$

From eqn (1)

$$1. \frac{dV(t)}{dt} + 10x \neq 0$$

$$\frac{dV(t)}{dt} = -\neq 0$$

$$dV = -\neq 0 = -k_1 e^{-t} - 3k_2 e^{-3t}$$

$$-k_1 - 3k_2 = -\neq 0 \quad \text{--- (3)}$$


Solving (2) and (3)

$$k_1 = -5 \quad k_2 = 15$$

$$\Rightarrow V(t) = -5e^{-t} + 15e^{-3t}$$

current Mag. Induct.  $I_{\text{ind.}} = \int_0^t (-5e^{-t} + 15e^{-3t}) dt$
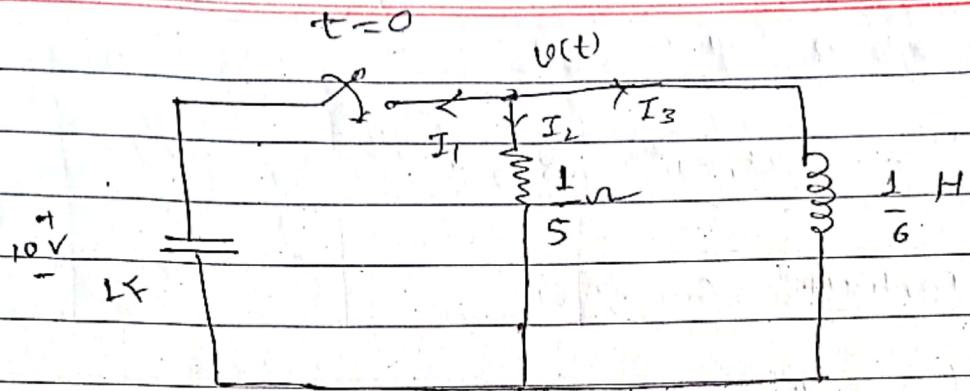
$$I(t)_{\text{ind.}} = 15e^{-t} - 135e^{-3t}$$



SQ At  $t=0$ , apply KCL.

$$I_1 + I_2 + I_3 = 0$$

$$\therefore \frac{d v(t)}{dt} + \frac{v(t)}{\frac{1}{5}} + \frac{1}{\frac{1}{6}} \int v(t) dt = 0 \quad \text{--- (1)}$$

Diff w.r.t  $t$ .

$$\frac{d^2 v(t)}{dt^2} + 5 \frac{d v(t)}{dt} + 6 v(t) = 0$$

Its char. eqn

$$m^2 + 5m + 6 = 0$$

$$m = -2, -3$$

$$\therefore v(t) = k_1 e^{-2t} + k_2 e^{-3t} \quad \text{--- (2)}$$

Initially,  $v(0) = 10V$  then,

$$10 = k_1 \times e^{-2 \times 0} + k_2 \times e^{-3 \times 0}$$

$$k_1 + k_2 = 10 \quad \text{--- (3)}$$

Diff eqn (2) w.r.t. to t

$$\frac{d u(t)}{dt} = -2k_1 e^{-2t} - 3k_2 e^{-3t} \quad (4)$$

now initialy for eqn (1)

$$\frac{d u(t)}{dt} + 5u(t) + 0 = 0$$

$$\frac{d u(t)}{dt} = -50$$

on general sol

then from (4)

$$-50 = -2k_1 e^{-2t} - 3k_2 e^{-3t}$$

$$-2k_1 - 3k_2 = -50 \quad (5)$$

solving (3) and (5) we get

$$k_1 = -20$$

$$k_2 = 80$$

Hence from (2)

$$u(t) = -20e^{-2t} + 80e^{-3t}$$









now current or inductor,  $i_{ind} = 6 \int u(t) dt$

$$i(t)_{ind} = 6 \int (-20e^{-2t} + 80e^{-3t}) dt$$


$$= 6 \{ 10e^{-2t} - 80e^{-3t} \}$$

$$= 270e^{-2t} - 570e^{-3t}$$


\* Calculation of initial values and their derivatives at  $t = 0^+$ .
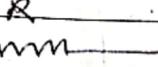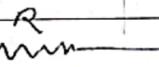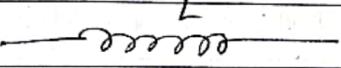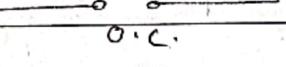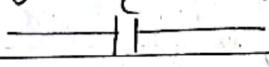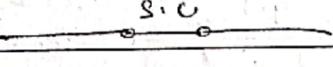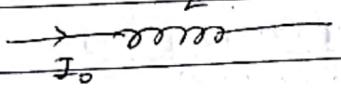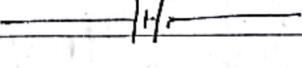
<u>Elements at <math>t = 0</math></u>	<u>Equivalent elements at <math>t = 0^+</math></u>
(1) Resistor 	(1) No change 
(2) Inductor with no initial current. 	(2) Acts as open circuit 
(3) Capacitor with no initial charge or voltage 	(3) Acts as short circuit 
(4) Inductor with initial current 	(4) Acts as current source $I_0$ 
(5) Capacitor with initial charge or voltage 	(5) Acts as voltage source  $Q_0 = CV_0$ $V_0 = \frac{Q_0}{C}$

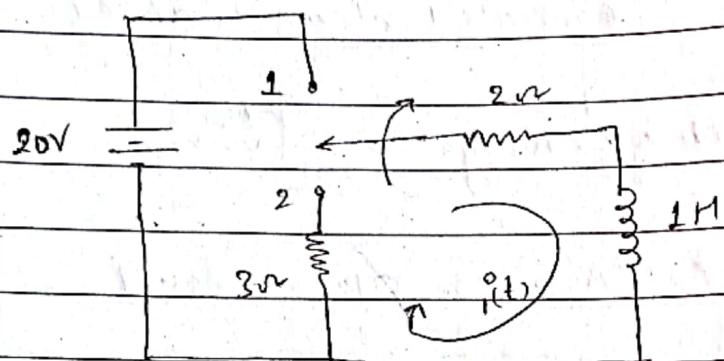
# Switch is moved from position 2 to position 1 at  $t = 0$ . Find  $i(t)$ ,  $\frac{di(t)}{dt}$  and  $\frac{d^2 i(t)}{dt^2}$  at  $t = 0^+$



At  $t = 0^+$

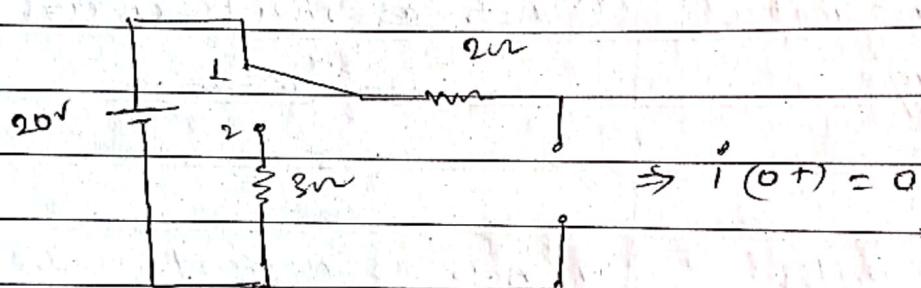

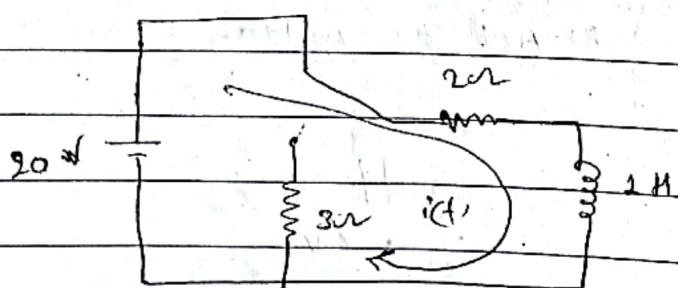To find derivatives, we consider original ckt at  $t = 0^-$



Apply KVL.

$$-2i(t) - 1 \cdot \frac{di(t)}{dt} + 20 = 0$$

$$2i(t) + \frac{di(t)}{dt} = 20$$

At  $t = 0^+$ ,

$$2i(0^+) + \frac{di(0^+)}{dt} = 20 \quad \text{--- (1)}$$

$$2 \times 0 + \frac{di(0^+)}{dt} = 20$$

$$\Rightarrow \frac{di(0^+)}{dt} = 20 \text{ A/s.}$$

S.t.d. eqn (1)

$$2 \frac{di(0^+)}{dt} + \frac{d^2 i(0^+)}{dt^2} = 0$$

$$2 \times 20 + \frac{d^2 i(0^+)}{dt^2} = 0$$


$$\Rightarrow \frac{d^2 i(0^+)}{dt^2} = -20 \text{ A/s}^2$$

# switch is moved from 1 to 2.

At  $t = 0^+$ ,


$$\frac{20V}{2\Omega} = 10A$$

$$I_0 = \frac{20}{2\Omega}$$

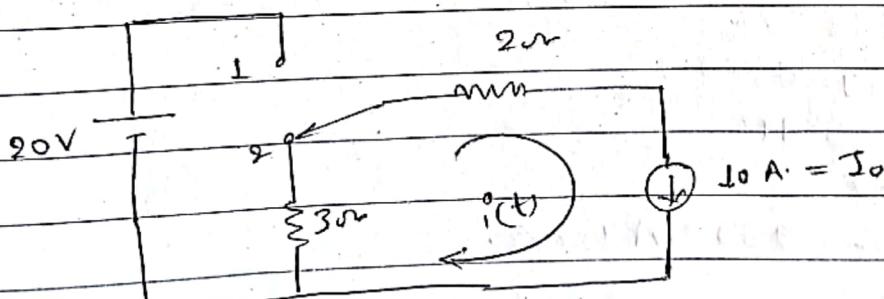

$$\Rightarrow i(0^+) = 10 \text{ A.}$$

To calculate derivatives.

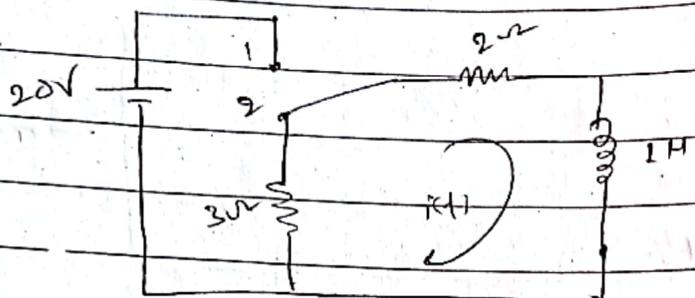

apply KVL,

$$-5i(0^+) - 1 \cdot \frac{di}{dt} = 0$$

$$\text{At } t = 0^+$$

$$5i(0^+) + 1 \cdot \frac{di(0^+)}{dt} = 0 \quad \text{--- (1)}$$

$$5 \times 10 + \frac{di(0^+)}{dt} = 0$$

$$\Rightarrow \frac{di(0^+)}{dt} = -50 \text{ A/sec}$$

Dif. (1)


$$5 \cdot \frac{di(0^+)}{dt} + 1 \cdot \frac{d^2i(0^+)}{dt^2} = 0$$

$$5 \times -50 + 1 \cdot \frac{d^2i(0^+)}{dt^2} = 0$$


$$\Rightarrow \frac{d^2i(0^+)}{dt^2} = 250 \text{ A/sec}^2.$$
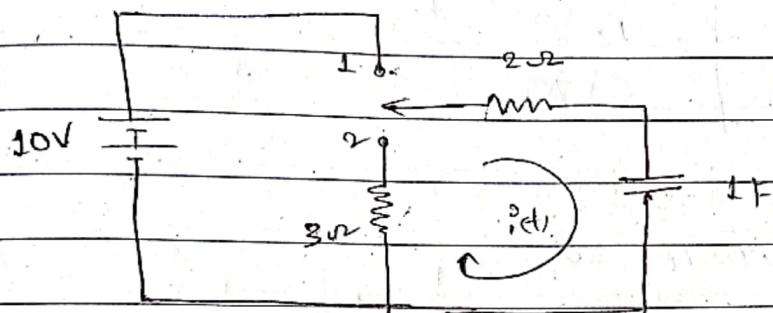
# switch is moved from position 1 to 2 at  $t=0$ .

Final  $i(t)$ ,  $\frac{di}{dt}$ , and  $\frac{d^2 i(t)}{dt^2}$  at  $t=0+$



At  $t=0+$ , equivalent circuit

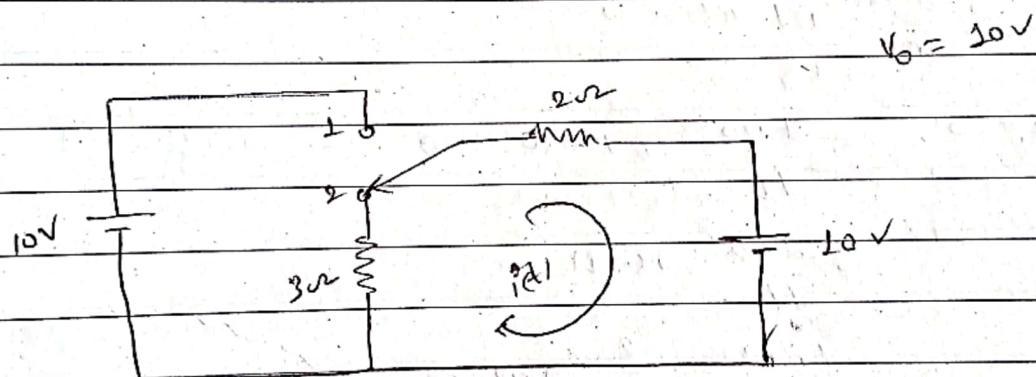

using KVL  $-5i(0+) - 10 = 0$


$$5i(0+) = -10$$

at  $t=0^+$

$$5i(0^+) = -10$$

$$\Rightarrow i(0^+) = -2 \text{ A.}$$

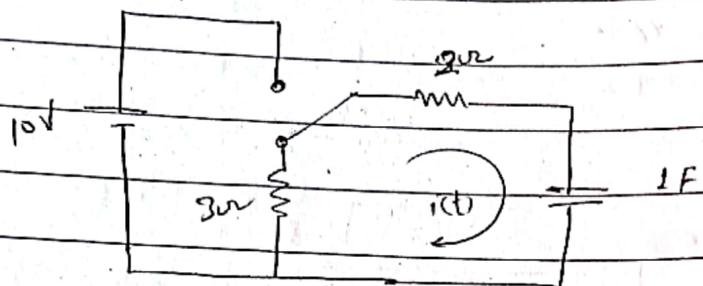To find derivatives, consider original  $i(t)$  at  $t = 0^+$ .



Applying KVL,

$$-3 \cdot i(t) - \frac{1}{2} \int i(t) dt = 0$$

$$5 \cdot i(t) + \frac{1}{2} \int i(t) dt = 0$$

Dif.

$$5 \frac{d i(t)}{dt} + 1 \cdot i(t) = 0$$

$$\text{At } t = 0^+, \quad 5 \frac{d i(0^+)}{dt} + 1 \cdot i(0^+) = 0 \quad \text{--- (1)}$$

$$5 \cdot \frac{d i(0^+)}{dt} + (-2) = 0$$

$$\Rightarrow \frac{d i(0^+)}{dt} = \frac{2}{5} \text{ Amp/sec.}$$

Again Dif (1)


$$5 \cdot \frac{d^2 i(0^+)}{dt^2} + \frac{d i(0^+)}{dt} = 0$$

$$5 \cdot \frac{d^2 i(0^+)}{dt^2} + \frac{2}{5} = 0$$


$$\Rightarrow \frac{d^2 i(0^+)}{dt^2} = -\frac{2}{25} \text{ Amp/sec}^2$$

H.W. From position 2 to 1. at  $t=0$ .

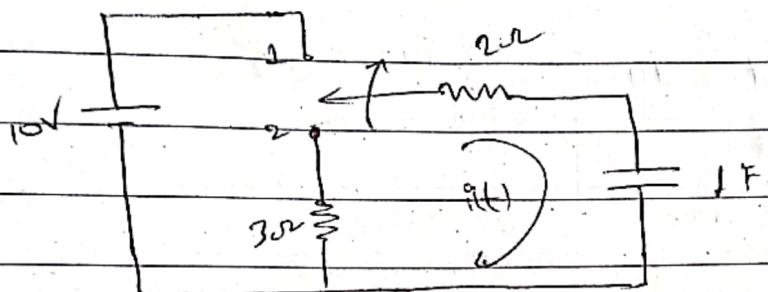Find  $i(t)$ ,  $\frac{di(t)}{dt}$ ,  $\frac{d^2 i(t)}{dt^2}$  at  $t=0+$




At  $t=0+$ , equivalent circuit.

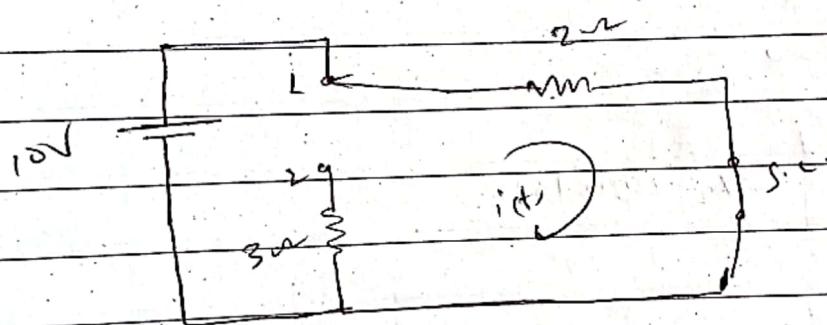

$$\Rightarrow i(t) = \frac{10}{2} = 5 \text{ Amp.}$$

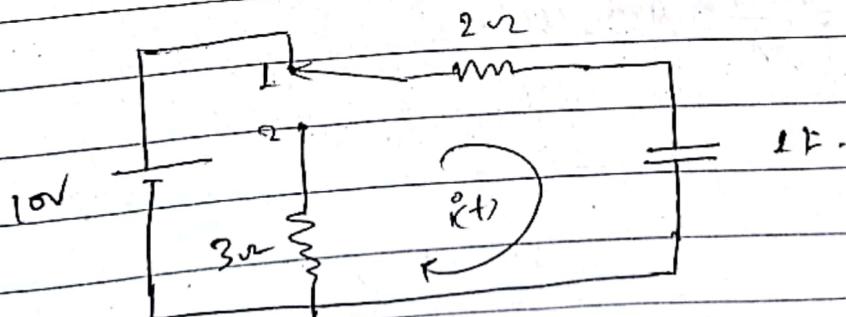To find derivatives,  
considering original circuit at  $t=0+$ .



Applying KVL,

$$-2 \overset{\circ}{i}(t) - \frac{1}{1} \int i(t) dt + 10 = 0$$

$$2 \overset{\circ}{i}(t) + \frac{1}{1} \int i(t) dt = 10 \quad \text{(1)}$$

D.T.F. (1)

$$2 \frac{d \overset{\circ}{i}(t)}{dt} + \overset{\circ}{i}(t) = 0$$

$$\text{at } t = (0^+)$$

$$2 \frac{d \overset{\circ}{i}(0^+)}{dt} + \overset{\circ}{i}(0^+) = 0 \quad \text{(2)}$$

$$2 \frac{d \overset{\circ}{i}(0^+)}{dt} + 5 = 0$$

$$\Rightarrow \frac{d \overset{\circ}{i}(0^+)}{dt} = -\frac{5}{2} \text{ Amp/sec.}$$

Again diff (1)


$$2 \cdot \frac{d^2 \overset{\circ}{i}(0^+)}{dt^2} + \frac{d \overset{\circ}{i}(0^+)}{dt} = 0$$

$$2 \frac{d^2 \overset{\circ}{i}(0^+)}{dt^2} - \frac{5}{2} = 0$$


$$\Rightarrow \frac{d^2 \overset{\circ}{i}(0^+)}{dt^2} = \frac{5}{4} \text{ Amp/sec.}$$

PV

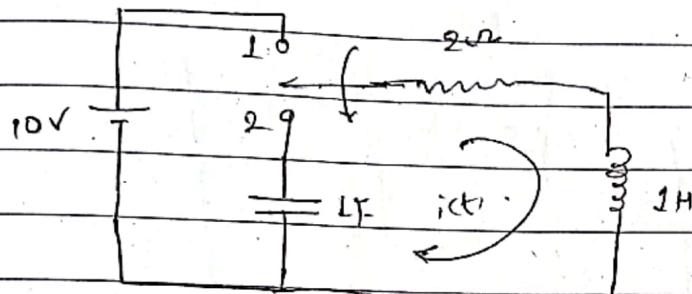
If switch is moved from position 1 to 2 at  $t=0$ .  
Find  $i(t)$ ,  $\frac{di(t)}{dt}$  and  $\frac{d^2 i(t)}{dt^2}$  at  $t=0^+$ .



At  $t=0^+$ , equivalent circuit

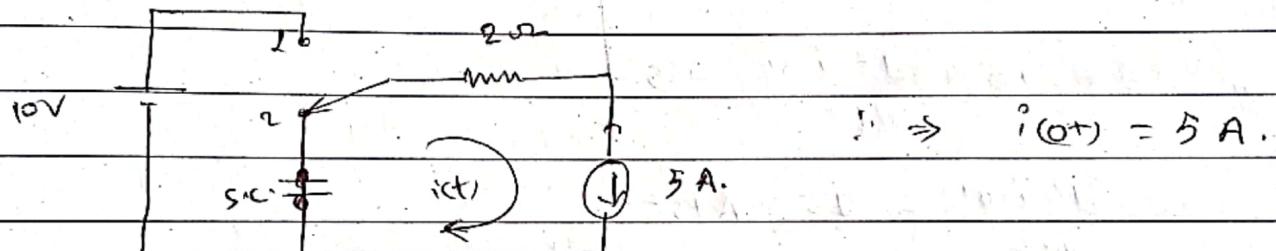

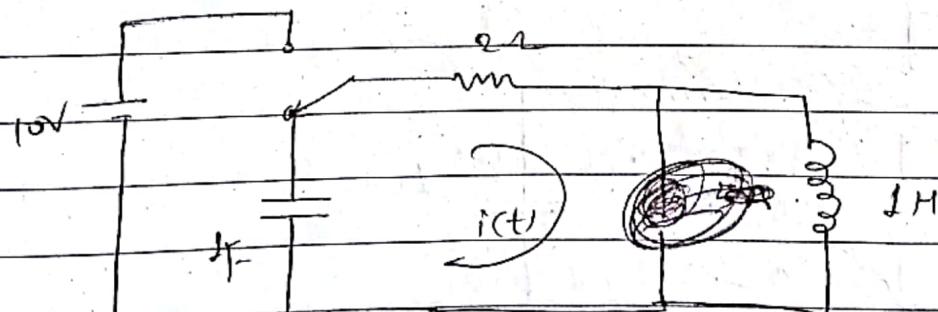To find derivatives, consider original ckt



Applying KVL,

$$-2i(t) - 1 \cdot \frac{di(t)}{dt} - \frac{1}{1} \int i(t) dt = 0$$

$$\therefore 2i(t) + \frac{di(t)}{dt} + \int i(t) dt = 0$$

At  $t = 0^+$

$$2i(0^+) + \frac{di(0^+)}{dt} + \int i(0^+) dt = 0 \quad \text{(1)}$$

$$2 \times 5 + \frac{di(0^+)}{dt} = 0$$

$$\Rightarrow \frac{di(0^+)}{dt} = -10 \text{ A/s}$$

Dif - (1)


$$2 \frac{d(i(0^+))}{dt} + \frac{d^2 i(0^+)}{dt^2} + i(0^+) = 0$$

$$2 \times -10 + \frac{d^2 i(0^+)}{dt^2} + 5 = 0$$

$$\Rightarrow \frac{d^2 i(0^+)}{dt^2} = 15 \text{ A/s}^2$$


~~Ao~~

same q'

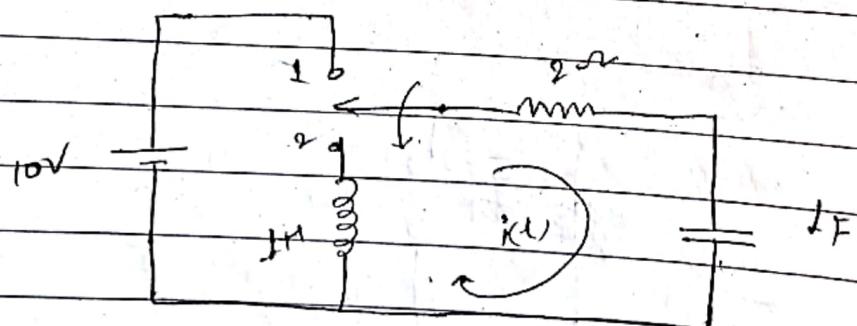


At  $t = 0^+$ , q' ckt.

$$\Rightarrow i(0^+) = 0 \text{ A.}$$

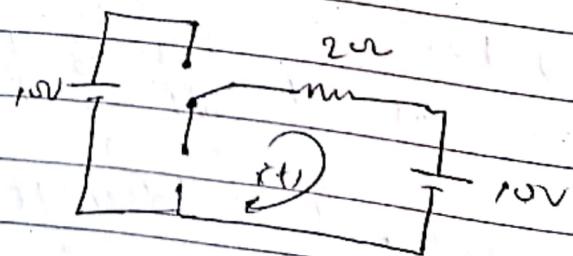

To find derivatives

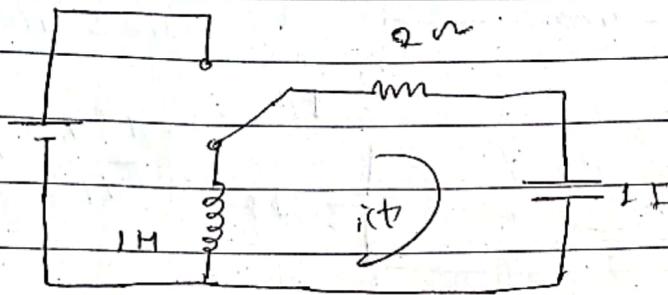

applying KVL,

$$2i(t) + 1 \cdot \frac{di(t)}{dt} + \frac{1}{1} \int i(t) dt = 0$$

$$\text{at } t = 0^+$$

$$2i(0^+) + \frac{di(0^+)}{dt} + 1 \cdot \int i(0^+) dt = 0 \quad \rightarrow 20V \quad \text{--- (1)}$$

$$2 \times 0 + \frac{di(0^+)}{dt} + 10 = 0$$

$$\Rightarrow \frac{di(0^+)}{dt} = -10 \text{ A/s}$$


diff. (1)

$$2 \frac{d^2 i(0^+)}{dt^2} + \frac{d^3 i(0^+)}{dt^3} + i(0^+) = 0$$

$$\therefore 2 \times -10 + \frac{d^2 i(0^+)}{dt^2} + 0 = 0$$

$$\Rightarrow \frac{d^2 i(0^+)}{dt^2} = 20 \text{ A/s}^2$$

H1W

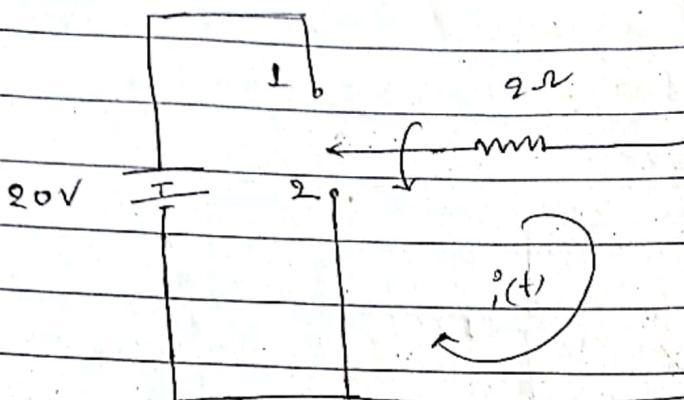


switch moved from 1 to 2

at  $t = 0^+$ Find  $i(0^+)$ ,  $\frac{di(0^+)}{dt}$ 

$$\frac{d^2i(0^+)}{dt^2}$$


OR, switch was at 1 for long time and the circuit reached to steady state before switching. Find ...

At  $t = 0^+$ , equivalent circuit,

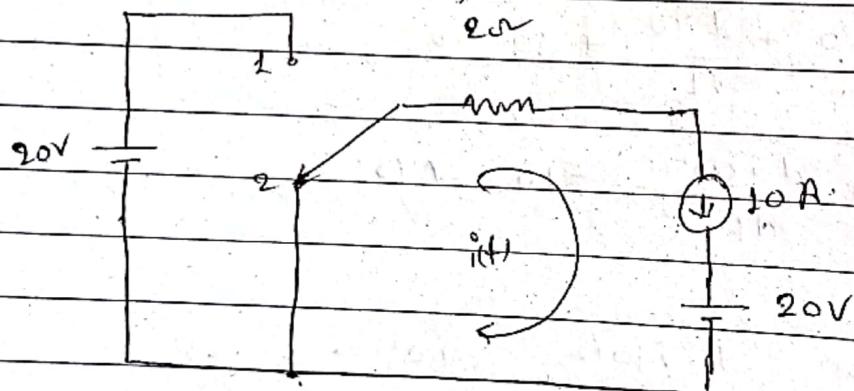

$$\Rightarrow i(0^+) = 10\text{ A} - \frac{20}{2}\text{ A} = 0\text{ A.}$$

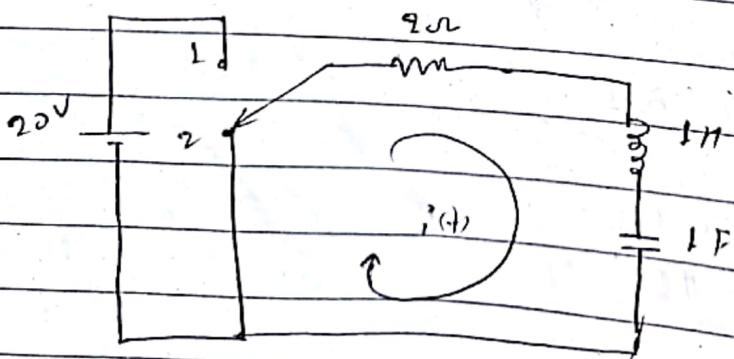To find derivatives, we consider original circuit at  $t = 0^+$



Apply KVL.

$$\textcircled{2} \quad 2i(t) + L \cdot \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt = 0$$

$$\textcircled{1}, \quad \cancel{2i(0^+)} = 0$$

$$\text{At } t = 0^+,$$

$$2i(0^+) + L \cdot \frac{di(0^+)}{dt} + \frac{1}{C} \int i(0^+) dt = 0 \quad \textcircled{1}$$

$$\textcircled{1} \quad 2 \times \textcircled{1} + \frac{di(0^+)}{dt} + 20 = 0$$

$$\Rightarrow \frac{di(0^+)}{dt} = -20 \text{ A/sec.}$$

Diff \textcircled{1} w.r.t.


$$2 \frac{d i(0^+)}{dt} + \frac{d^2 i(0^+)}{dt^2} + i(0^+) = 0$$

$$\textcircled{1} \quad 2 \times -20 + \frac{d^2 i(0^+)}{dt^2} + \textcircled{1} = 0$$


$$\Rightarrow -40 + \frac{d^2 i(0^+)}{dt^2} + \textcircled{1} = 0$$

$$\Rightarrow \frac{d^2 i(0^+)}{dt^2} = 40 \text{ A/sec}^2$$

For the network shown below, the switch K is opened at  $t=0$ . Find  $v(t)$ ,  $\frac{dv(t)}{dt}$  and  $\frac{d^2v(t)}{dt^2}$  at  $t=0^+$

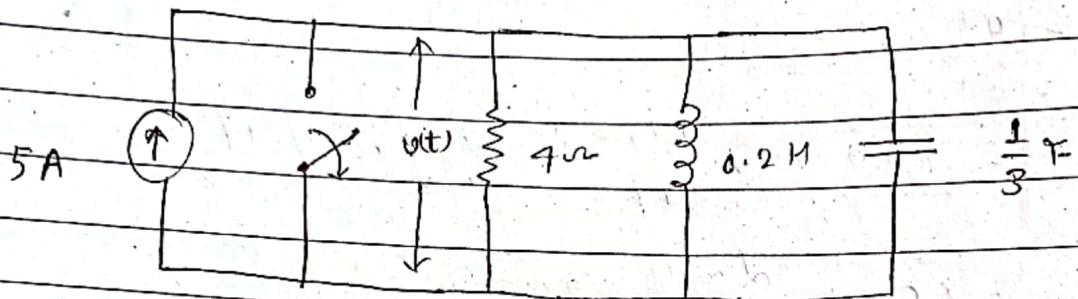
 $\text{so } v^n$ 

At  $t=0^+$ , equivalent circuit is

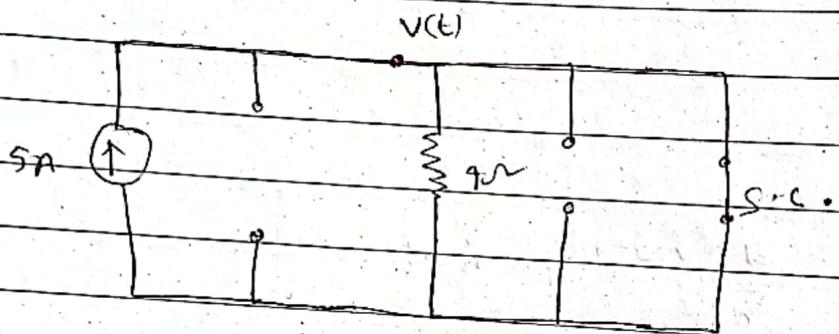

$$v(0^+) = 0 \text{ V} \quad (\text{Due to short circuit})$$

To find derivatives,

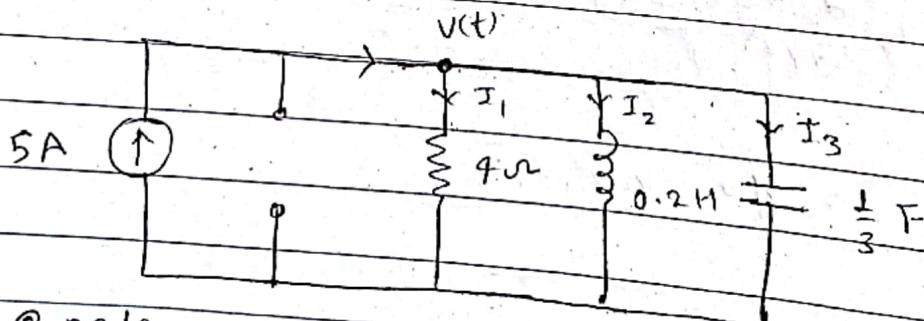

KCL @ node,

$$I_1 + I_2 + I_3 = 5$$

$$\frac{v(t)}{4} + \frac{1}{0.2} \int v(t) dt - \frac{1}{3} \frac{dv(t)}{dt} = 5$$

At  $t = 0^+$ ,

$$\frac{1}{4} v(0^+) + \frac{1}{0.2} \int_0^{0^+} v(t) dt + \frac{1}{3} \frac{d v(0^+)}{dt} = 5 \quad (1)$$

$$0 + 0 + \frac{1}{3} \frac{d v(0^+)}{dt} = 5$$

$$\Rightarrow \frac{d v(0^+)}{dt} = 15 \text{ V/s}$$


Diff eq ①

$$\frac{1}{4} \frac{d v(0^+)}{dt} + \frac{1}{0.2} v(0^+) + \frac{1}{3} \frac{d^2 v(0^+)}{dt^2} = 0$$

$$\Rightarrow \frac{1}{4} \times 15 + \frac{1}{0.2} \times 0 + \frac{1}{3} \frac{d^2 v(0^+)}{dt^2} = 0$$


$$\Rightarrow \frac{d^2 v(0^+)}{dt^2} = -\frac{45}{4} \text{ V/s}^2$$

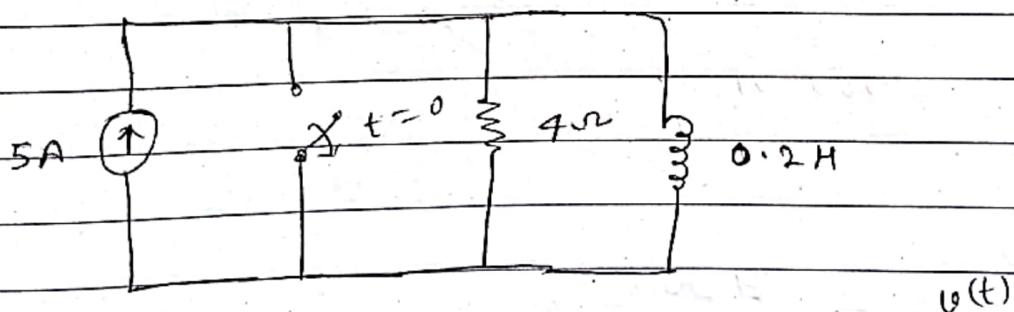Find  $v(t)$ ,  $\frac{d v(t)}{dt}$  &  $\frac{d^2 v(t)}{dt^2}$  at  $t = (0^+)$




At  $t = 0^+$ , eq 1st. is
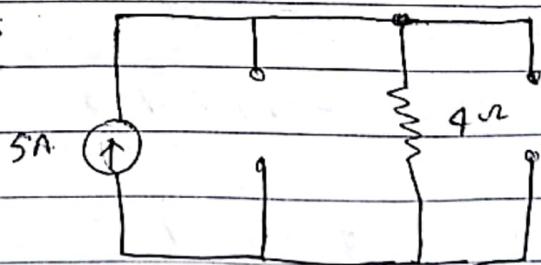
$$\begin{aligned} v(0^+) &= 5 + 4 \\ &= 20 \text{ V} \end{aligned}$$



To find derivatives,

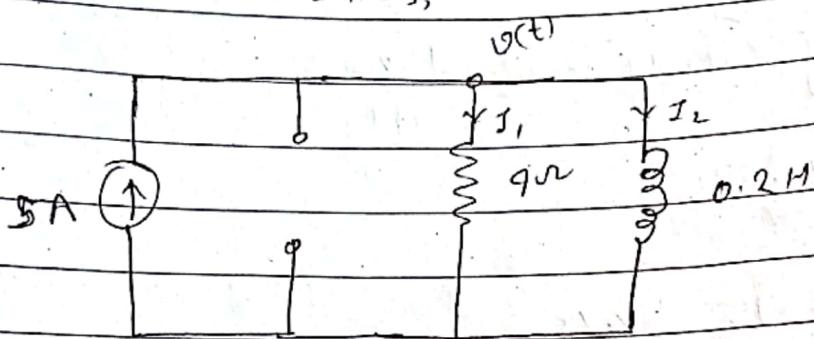

At node, applying KCL.

$$I_1 + I_2 = 5$$

$$\frac{V(t)}{9} + \frac{1}{0.2} \int V(t) dt = 5$$

at  $t = 0^+$ ,

$$\frac{V(0^+)}{9} + \frac{1}{0.2} \int V(0^+) dt = 5$$

Dif. w.r.t.  $t$ ,

$$\frac{1}{9} \frac{d V(0^+)}{dt} + \frac{1}{0.2} V(0^+) = 0 \quad (1)$$

$$\frac{1}{9} \frac{d V(0^+)}{dt} = -5 \times 20$$

$$\frac{d V(0^+)}{dt} = -900 \text{ V/s.}$$

Dif. (1)

$$\frac{1}{9} \frac{d^2 V(0^+)}{dt^2} + \frac{1}{0.2} \frac{d V(0^+)}{dt} = 0$$

$$\frac{1}{9} \frac{d^2 V(0^+)}{dt^2} = -5 \times -900$$

$$\frac{d^2 V(0^+)}{dt^2} = 8000 \text{ V/s}^2$$